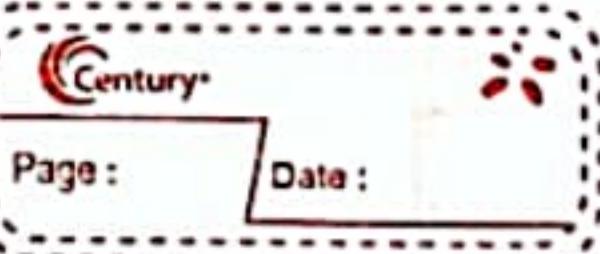


# Electricity and Magnetism


## ELECTRICAL CIRCUITS




### \* KIRCHHOFF's LAW
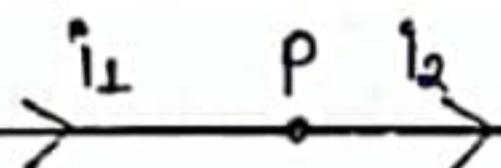
#### 1. Kirchhoff's First Law

Kirchhoff's first law states that, "The sum of the current entering any point in the circuit is equal to the sum of the current leaving the same point."



Fig(i)

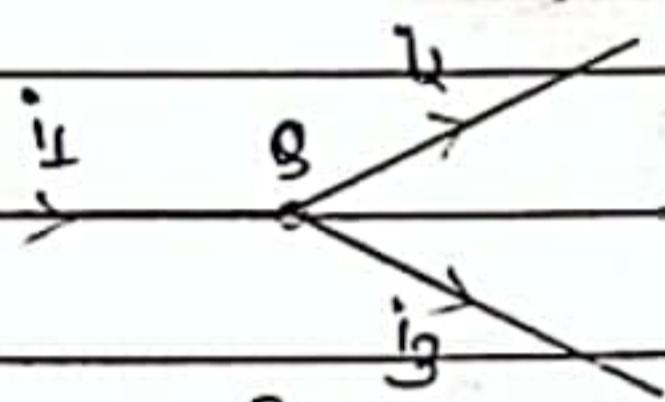

Fig(ii)

Fig: Kirchhoff's first law

In Fig(ii), the current into point P must equal the current out. So,  
 $i_1 = i_2 + i_3$ .

In Fig(ii), one current is entering into point Q and two currents leaving. The current gets divided at Q. So,

$$i_1 = i_2 + i_3$$


Kirchhoff's first law is an expression of conservation of charge. The idea is that the total amount of charge entering a point must exit the point. Kirchhoff's first law can be written as:

$$\sum I_{in} = \sum I_{out}$$

where,  $\sum I_{in}$  = sum of all currents entering into a point.

$\sum I_{out}$  = sum of all currents leaving that point.

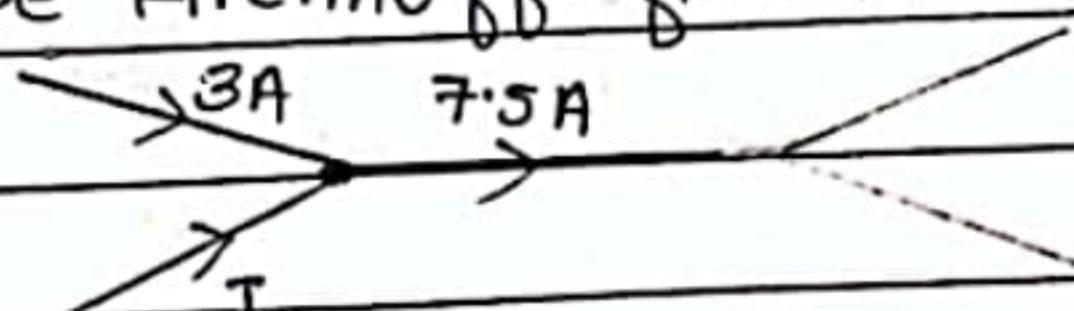Q1) Use Kirchhoff's first law to deduce the value of the current I.




Solution:

$$I + 3 = 7.5$$

$$I = 4.5A$$

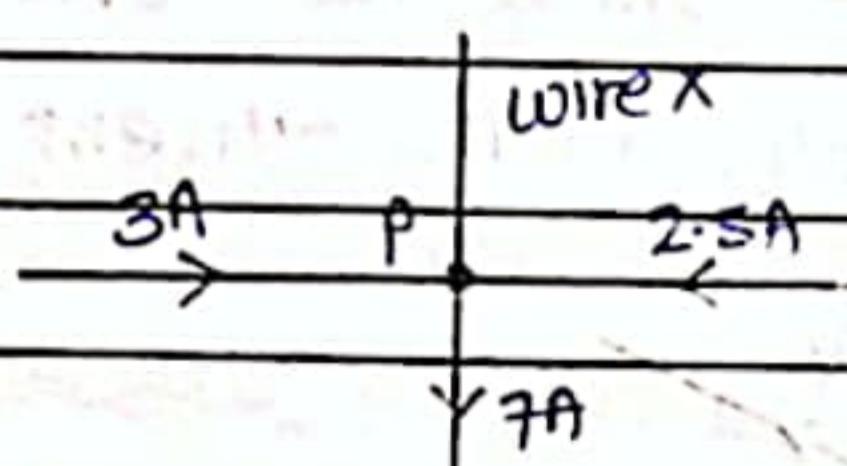Q2) Calculate the current in the wire X. State the direction of this current (towards P or away from P).



Solution:


Let, current in wire X be  $I$ .

$$\text{Then, } I + 7 = 3 + 2.5$$

$$\text{or, } I = -1.5 \text{ A}$$

$\therefore$  The current in wire X is  $1.5 \text{ A}$  towards P.

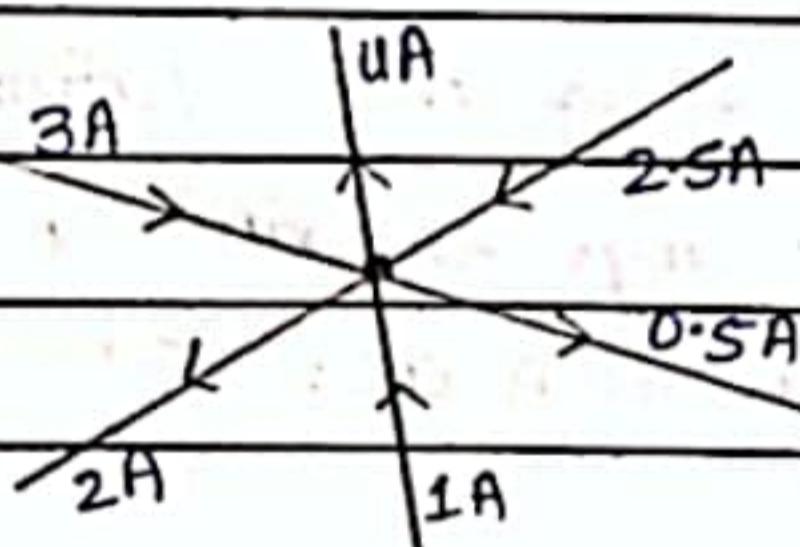Q3) Calculate  $\sum I_{\text{in}}$  and  $\sum I_{\text{out}}$  in the figure. Is Kirchhoff's first law satisfied.




Solution:

$$\sum I_{\text{in}} = 2.5 + 1 + 3 = 6.5 \text{ A}$$

$$\sum I_{\text{out}} = 4 + 0.5 + 2 = 6.5 \text{ A}$$

As  $\sum I_{\text{in}} = \sum I_{\text{out}}$ , Kirchhoff's first law is satisfied.

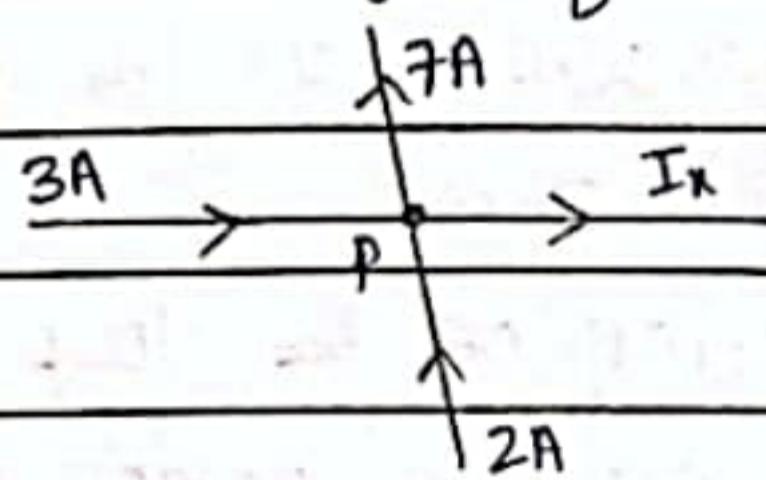34) Use Kirchhoff's first law to deduce the value and direction of current  $I_x$ .



Solution:

$$I_x + 7 = 3 + 2$$


$$\therefore I_x = -2A$$

$\therefore$  The value of current  $I_x$  is 2A towards P.
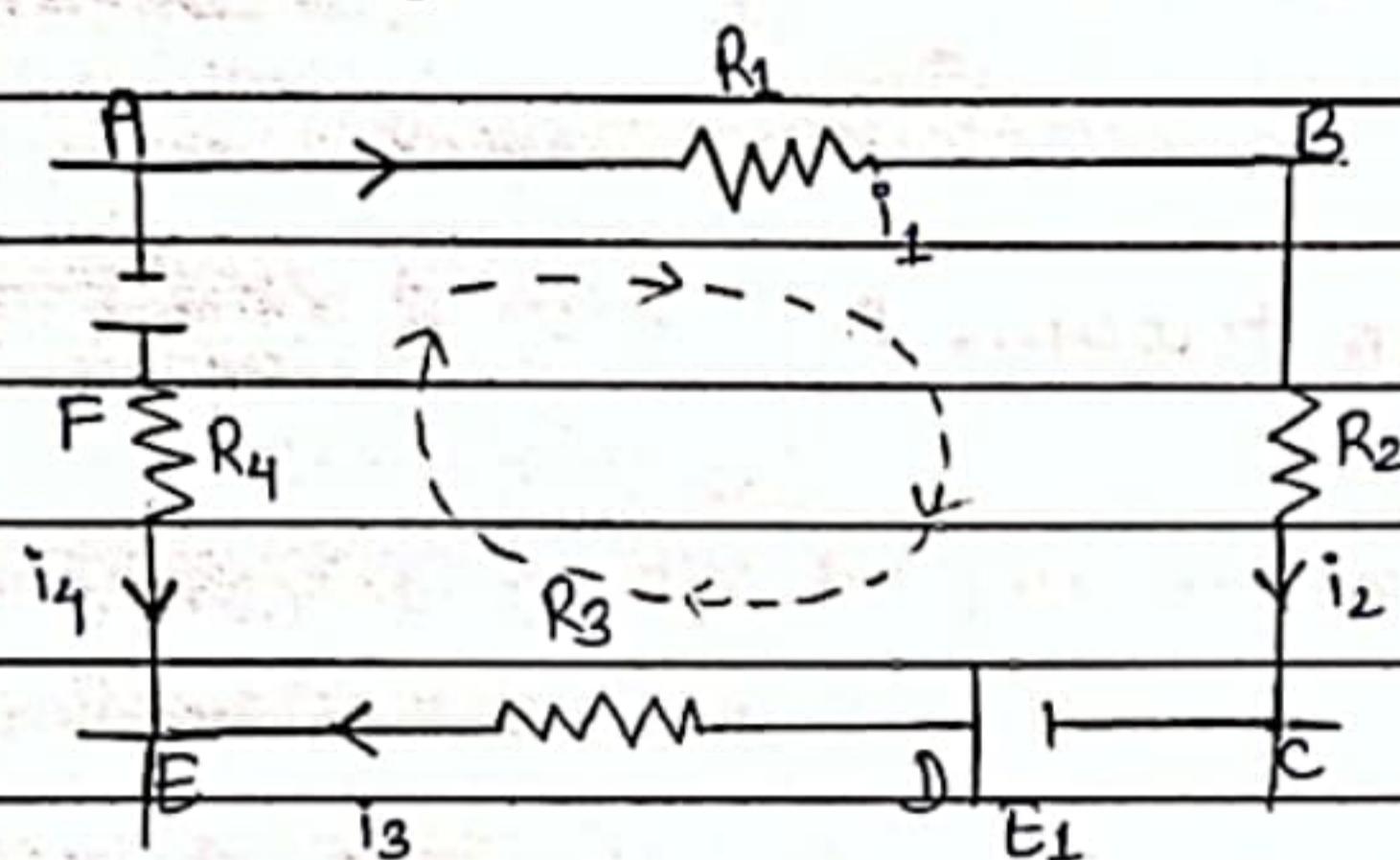
## 2. Kirchhoff's Second Law

Kirchhoff's Second Law states, "The algebraic sum of all the potential differences along a closed loop in a circuit is zero."

While using this rule, one starts from a point on the loop and goes along the loop to reach the same point. Any potential drop is taken negative and potential gain is taken positive.



In the figure, considering  $\text{ABCDEF}$  a loop, we get the following potential differences.

$$V_A - V_B = -i_1 R_1$$

$$V_B - V_C = -i_2 R_2$$

$$V_C - V_D = E_1$$

$$V_D - V_E = -i_3 R_3$$

$$V_E - V_F = i_4 R_4$$

$$V_F - V_A = -E_2$$

Adding all these,

$$0 = -i_1 R_1 - i_2 R_2 + E_1 - i_3 R_3 + i_4 R_4 - E_2$$

$$\therefore \sum \Delta V = 0$$


where  $\Delta V$  = potential differences along a closed loop.

Kirchhoff's second law is an expression of the conservation of energy.

It follows directly from the fact that electrostatic force is conservative force and work done by it in any closed path is zero.

## APPLYING KIRCHHOFF'S LAW

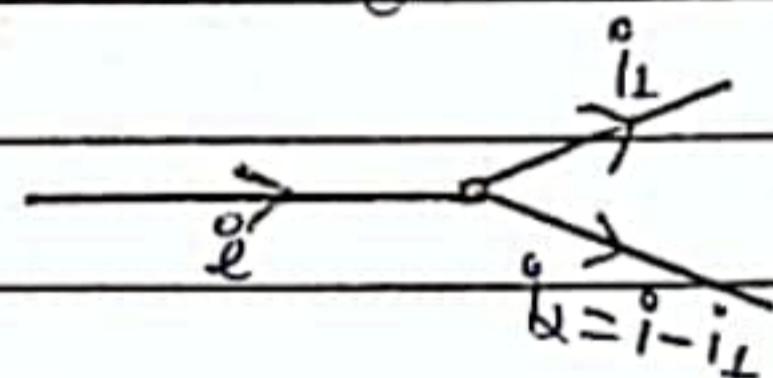1. Draw current from one or more cell. Follow Kirchhoff's current law (KCL) for distribution of current at junctions.



### 2. Choosing Loop(s)

- i. It/They must be closed loop/loops.
- ii. It/They can involve any number of cells, resistors, etc.

### 3. Direction of Loop / Path



The loop(s) can either be clockwise or anticlockwise but must be closed loop.

### 4. Potential drop or Potential gain



Higher Potential → Potential drop  
 ΔV = negative

Lower Potential → Potential gain  
 ΔV = positive

#### i. For cell

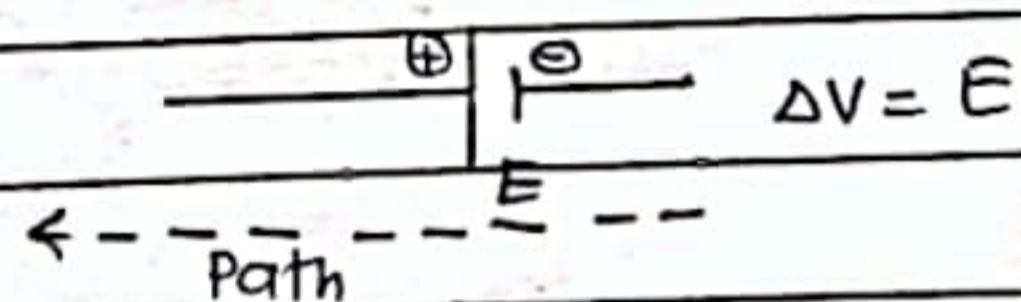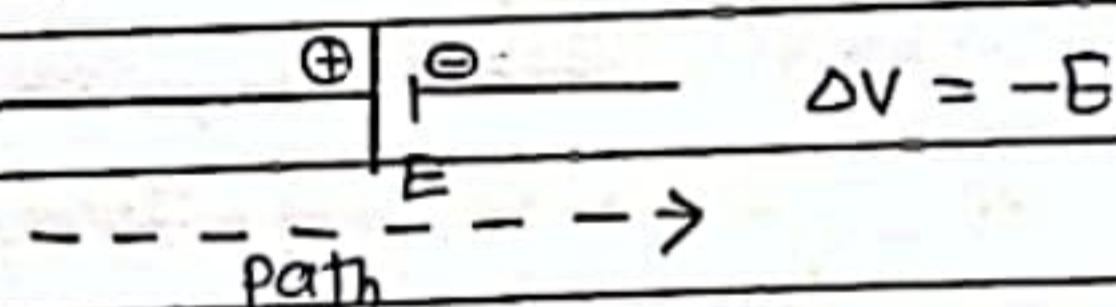


#### ii. For Resistor

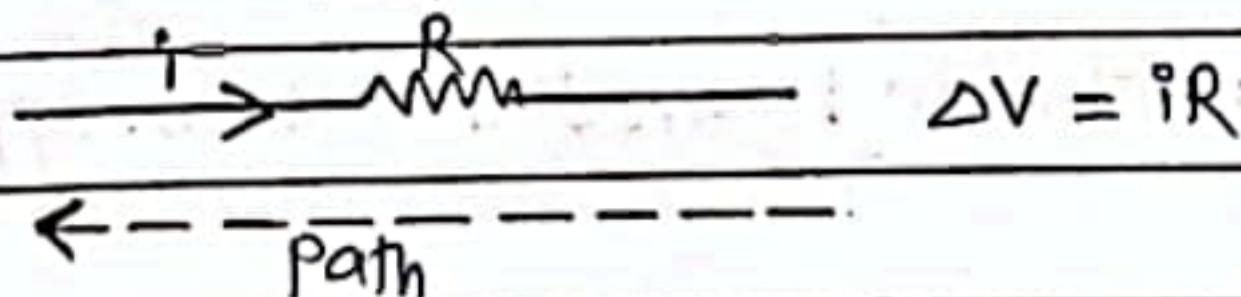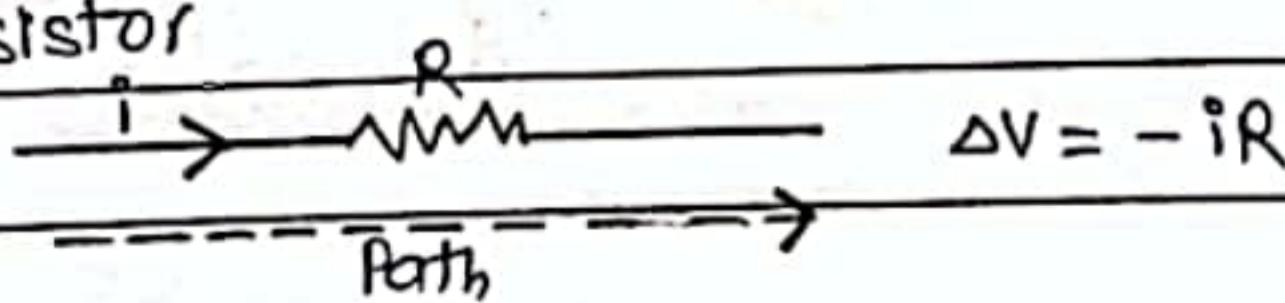


Q1 Find current in each resistor.

i)

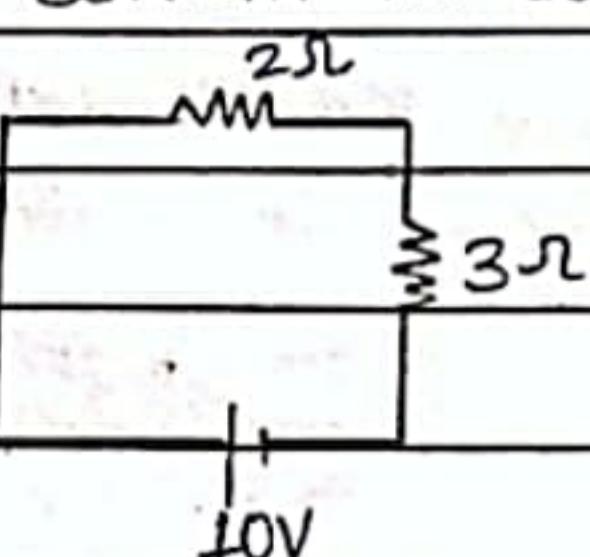

Solution:

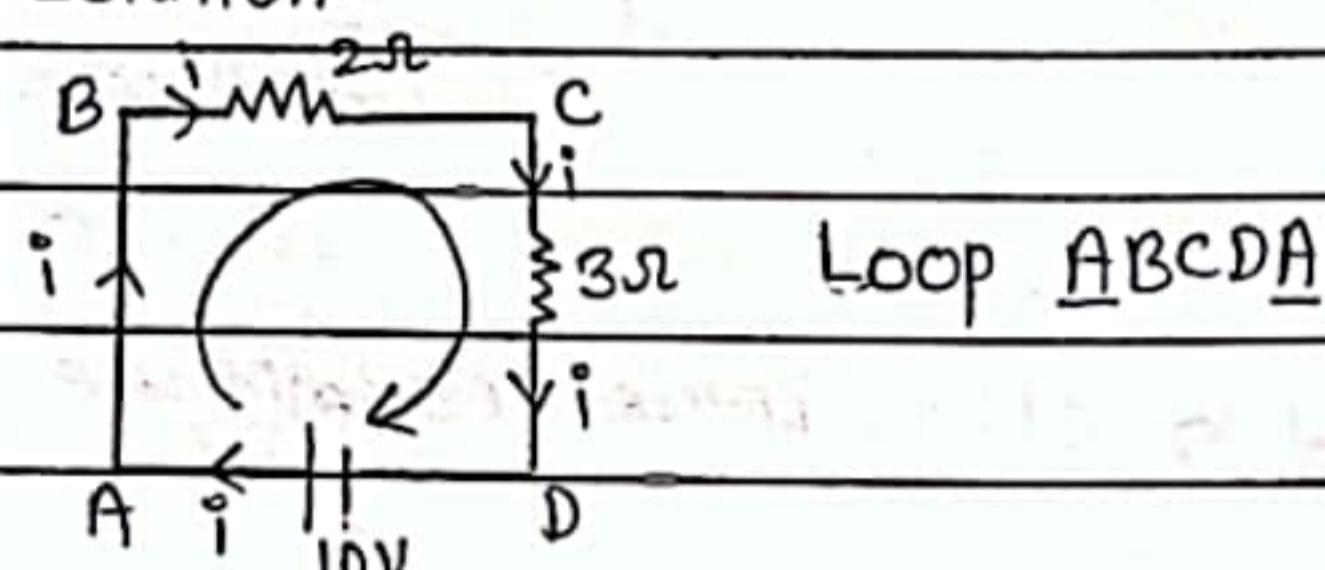


Suppose the current is  $i$  in the indicated direction. Applying Kirchhoff's loop law,

$$-2i - 3i + 10 = 0$$


$$5i = 10$$

$$\therefore i = 2 \text{ A}$$

ii)

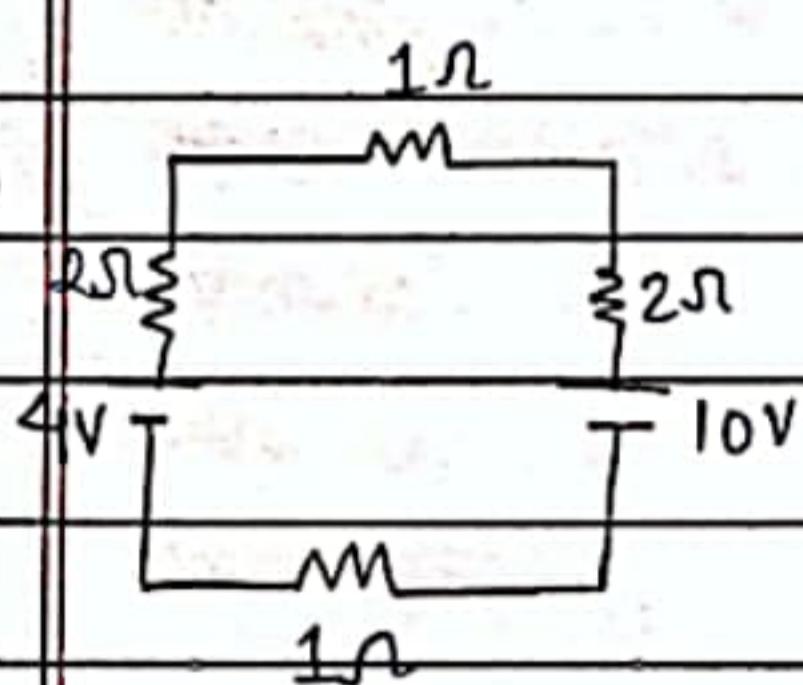

Solution:

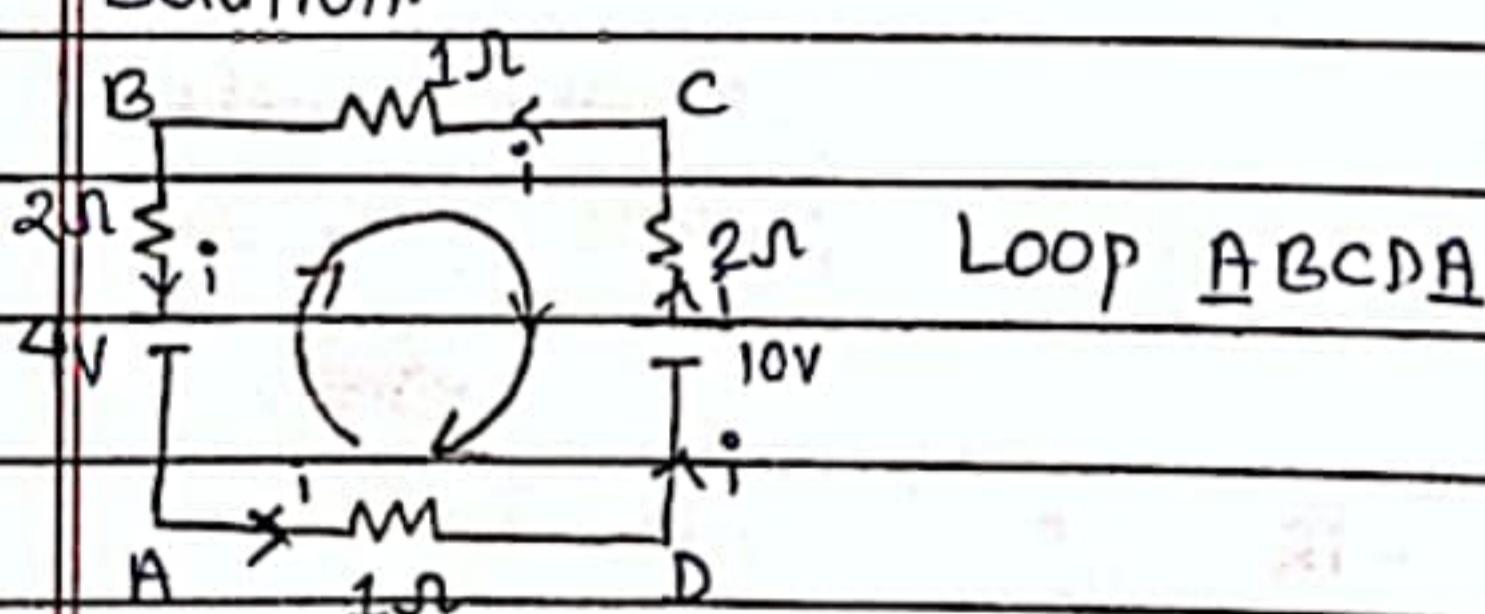


Suppose the current is  $i$  in the indicated direction. Applying Kirchhoff's loop law,


$$4 + 2i + i + 2i - 10 + i = 0$$

$$\text{or, } 6i = 6$$

$$\therefore i = 1 \text{ A}$$

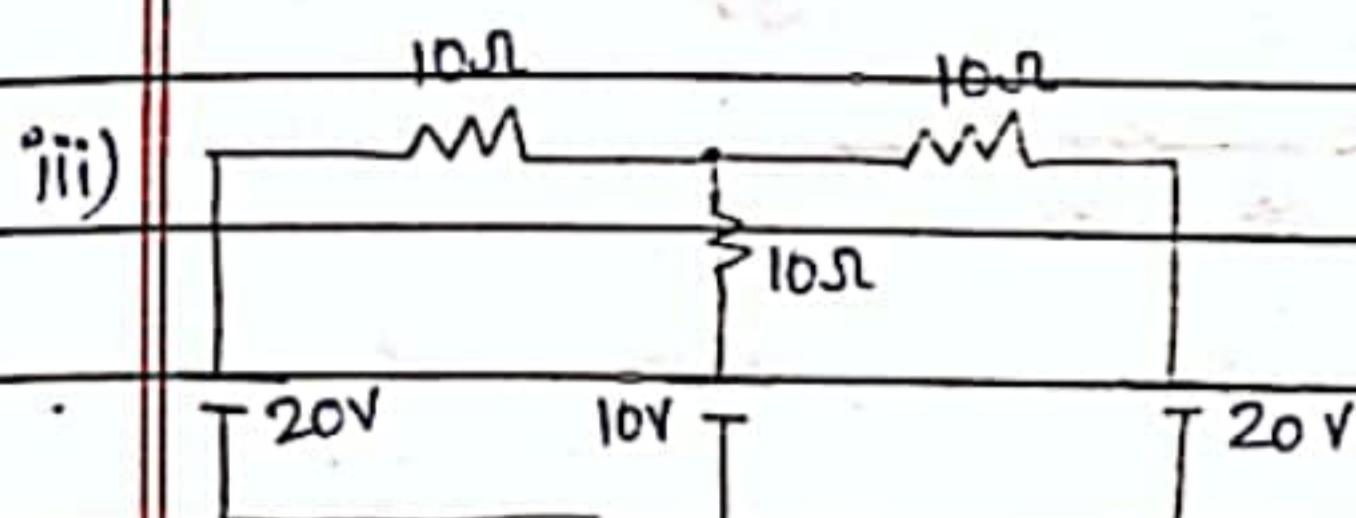

Solution:

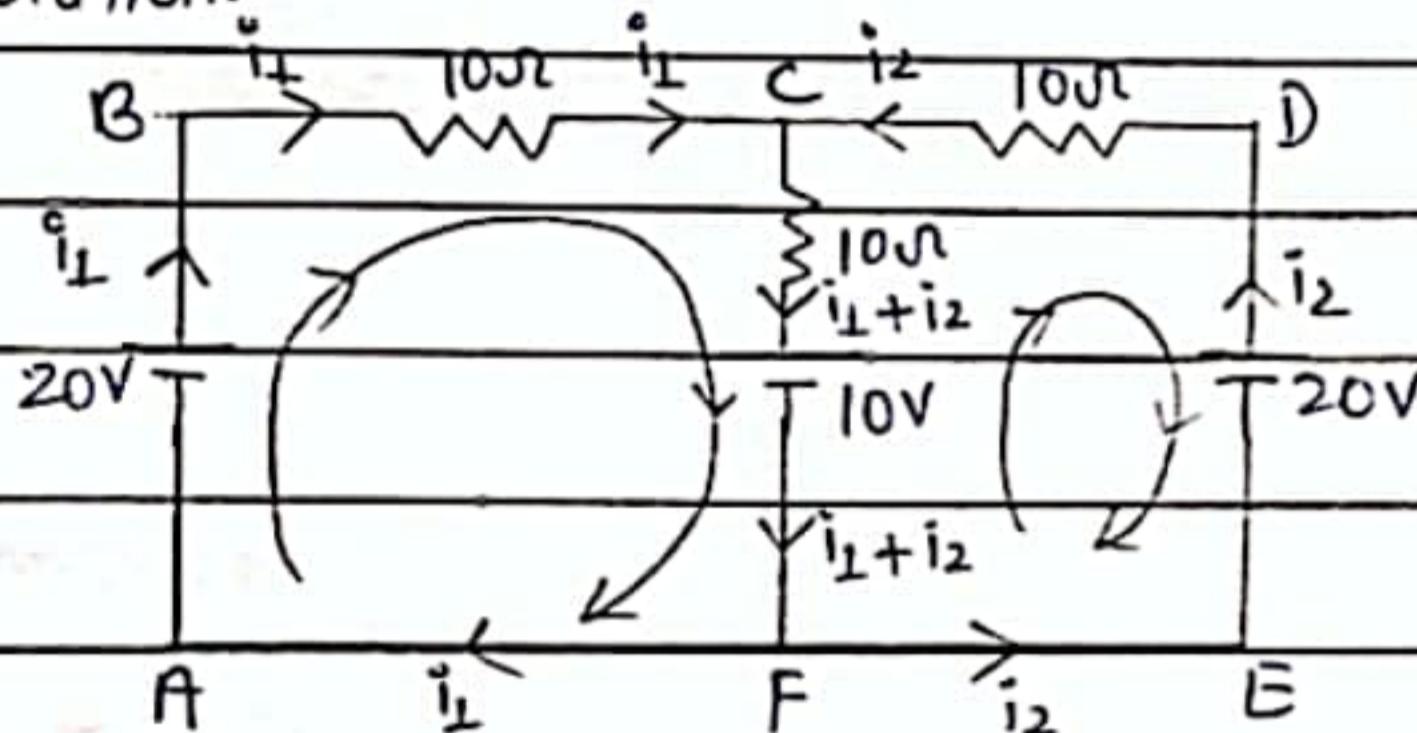

Suppose the current is  $i_1$  and  $i_2$  in the indicated direction.

Considering the loop ABCFA,

$$20 - 10i_1 - 10(i_1 + i_2) - 10 = 0$$

$$10 - 10i_1 - 10i_1 - 10i_2 = 0$$

$$2i_1 + i_2 = 1 \quad \text{--- (i)}$$

Considering the loop CDEFCA,

$$10 + 10(i_1 + i_2) + 10i_2 - 20 = 0$$

$$10 + 10i_1 + 20i_2 = 0$$

$$i_1 + 2i_2 = -1 \quad \text{--- (ii)}$$


Solving (i) and (ii),

$$i_1 = \frac{1}{3} \text{ A}, \quad i_2 = \frac{1}{3} \text{ A}$$


$$\therefore i_1 + i_2 = \frac{2}{3} \text{ A}$$

Q2. Find the current in  $1\Omega$  resistor.

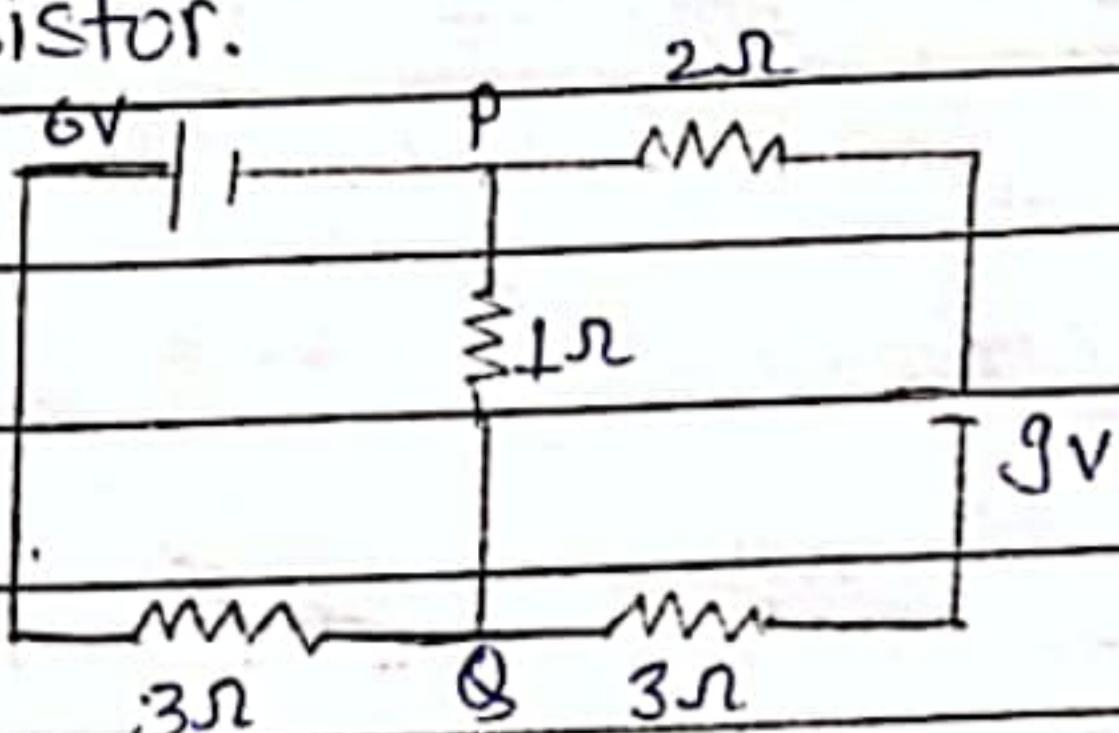- a)  $1.13A$   $P \rightarrow Q$
- b)  $1.13A$   $Q \rightarrow P$
- c)  $0.13A$   $Q \rightarrow P$
- d)  $0.13A$   $P \rightarrow Q$



Solution:

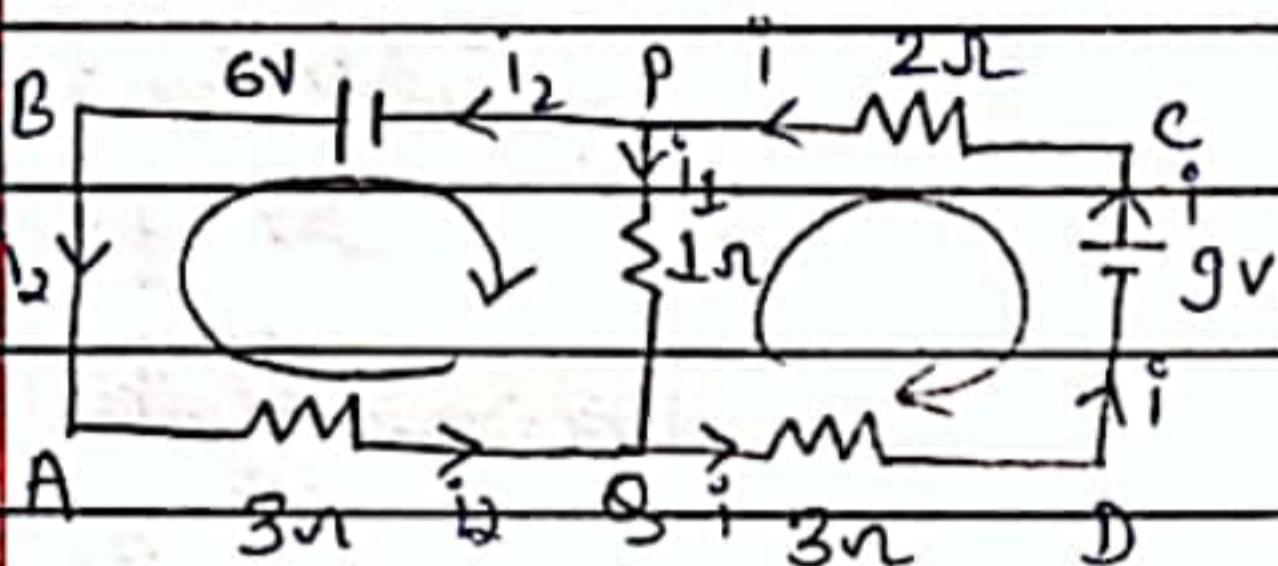

Considering loop ABCDA

$$3i_2 - 6 - i_1 = 0$$

$$3i_2 - i_1 = 6 \quad \text{--- (i)}$$

Considering loop CDQPC,

$$-9 + 3i + i_2 + 2i = 0$$

$$\text{or, } 5(i_1 + i_2) + i_1 = 9$$


$$\text{or, } 6i_1 + 5i_2 = 9 \quad \text{--- (ii)}$$

Solving (i) and (ii)


$$i_1 \approx -0.13A$$

Q3) Find current in each resistor.

- a) 0.25A
- b) 0.5A
- c) 0A
- d) 0.75A

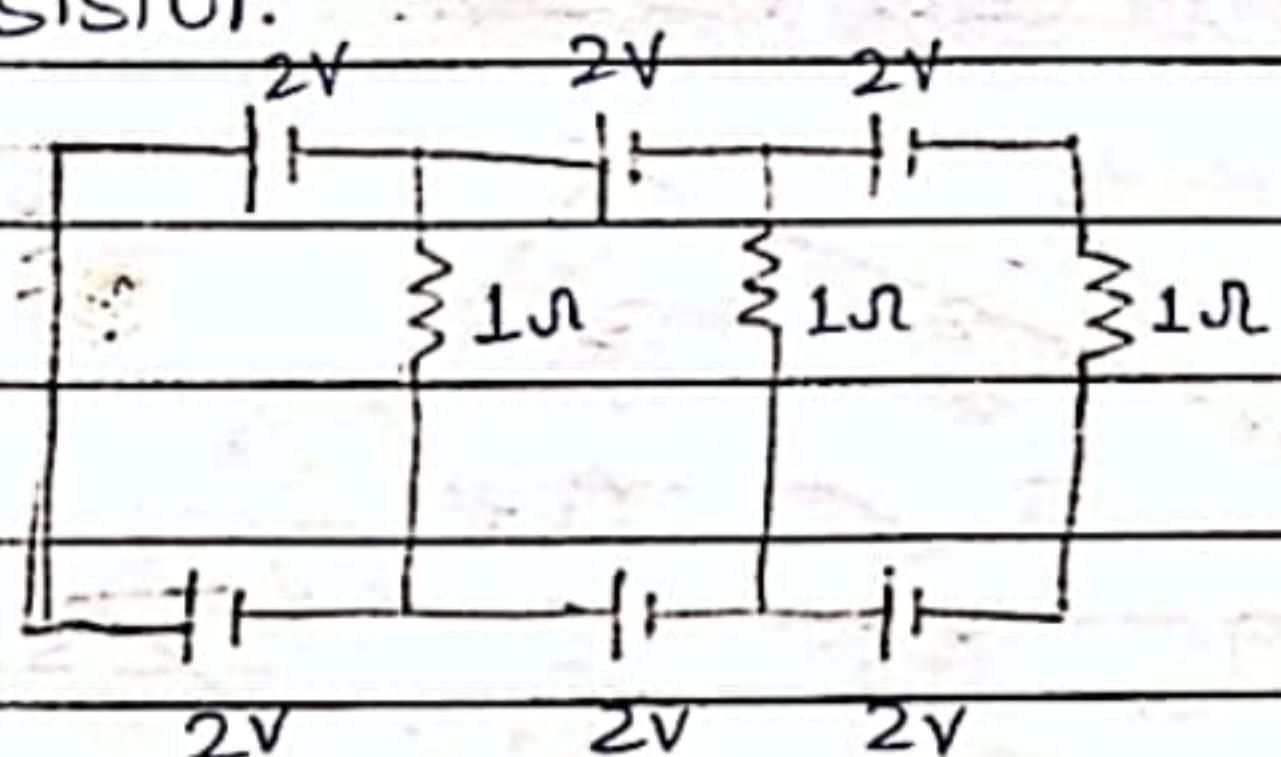

Solution:

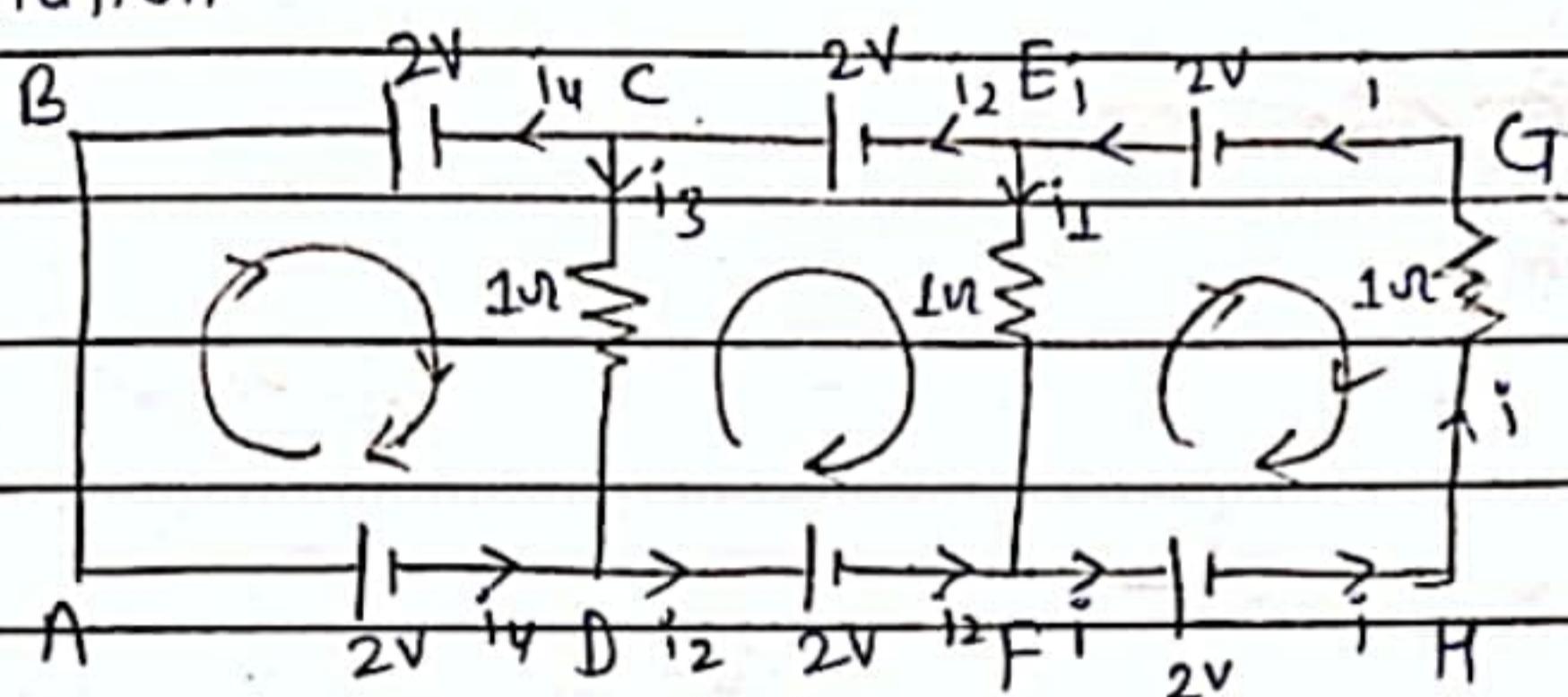

Considering loop ABCDA

$$2 - 2 - i_3 = 0$$

$$i_3 = 0A$$

Considering loop CEDFC

$$2 + i_3 - 2 - i_1 = 0$$

$$i_3 = i_1 = 0A$$


Considering loop EGHFE

$$2 + i_1 - 2 + i = 0$$

$$i = 0A$$

Q4)

Find current in each resistor.

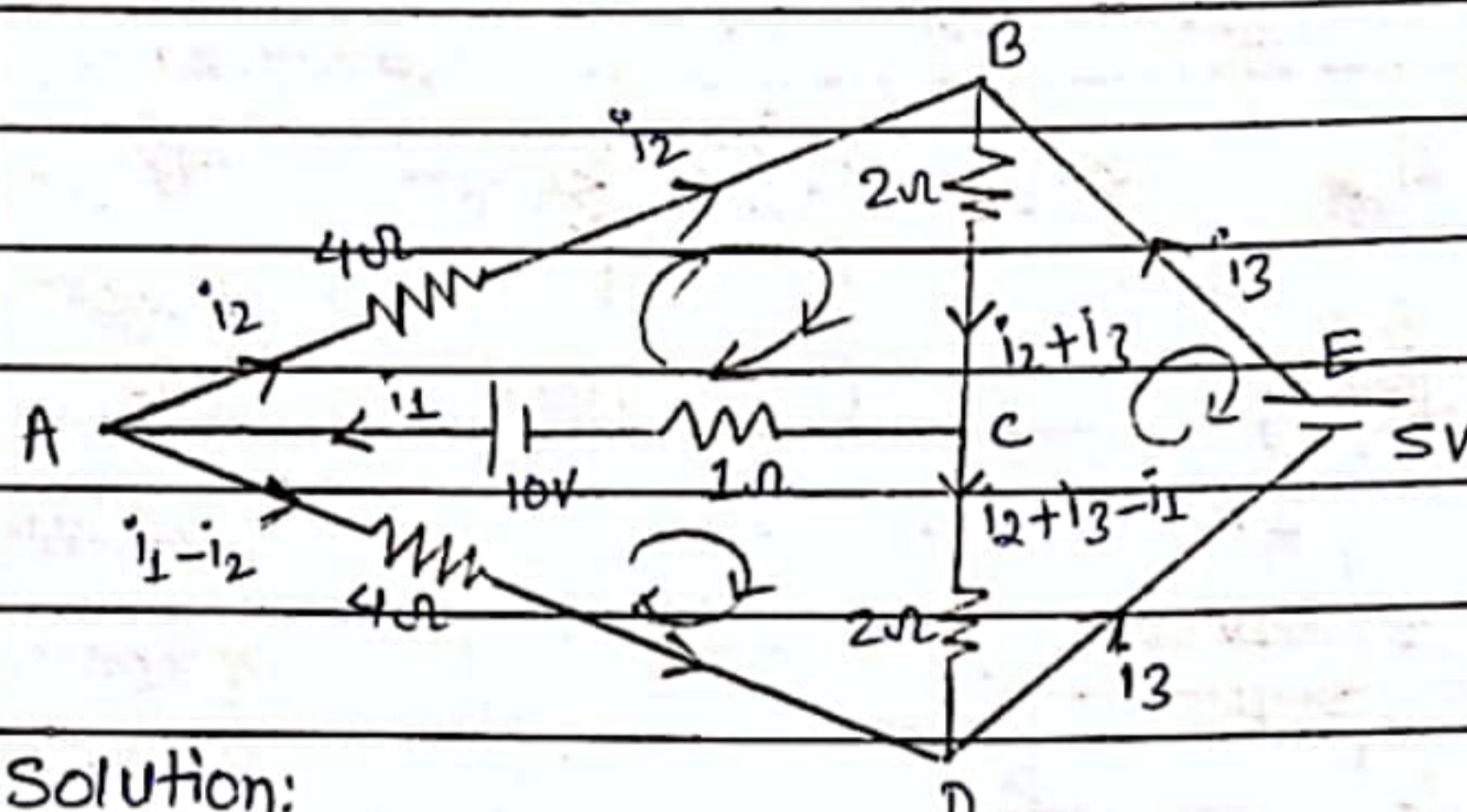

Solution:

For loop ABCA

$$10 - 4i_2 - 2i_2 - 2i_3 - i_1 = 0$$

$$10 - 6i_2 - 2i_3 - i_1 = 0$$

$$\textcircled{i} \quad i_1 + 6i_2 + 2i_3 = 10 \quad \dots \text{--- (i)}$$

For loop ACDA

$$-10 + i_1 - 2i_2 - 2i_3 + 2i_1 + 4i_1 - 4i_2 = 0$$

$$\textcircled{ii} \quad 7i_1 - 6i_2 - 2i_3 = 10 \quad \dots \text{--- (ii)}$$

For loop BEDB,

$$-5 + 2i_2 + 2i_3 - 2i_1 + 2i_2 + 2i_3 = 0$$

$$4i_2 + 4i_3 - 2i_1 = 5 \quad \dots \text{--- (iii)}$$

Adding (i) and (ii)

$$8i_1 = 20$$

$$i_1 = \frac{20}{8} = \frac{5}{2} \text{ A} = 2.5 \text{ A} \quad \dots \text{--- (iv)}$$

From (iv) and (i) &amp; (ii) and (iii) and (iv)

$$6i_2 + 2i_3 = 7.5 \quad \dots \text{--- (v)}$$

$$4i_2 + 4i_3 = 10 \quad \dots \text{--- (vi)}$$

Solving (v) and (vi),

$$i_2 = \frac{5}{8} = 0.625 \text{ A} \text{ and } i_3 = \frac{15}{8} = 1.875 \text{ A}$$

$\therefore$  Current in each resistor situated at

$$AB = i_2 = 0.625 \text{ A}$$

$$BC = i_2 + i_3 = 0.625 + 1.875 = 2.5 \text{ A}$$



$$CD = i_2 + i_3 - i_1 = 0.625 + 1.875 - 2.5 = 0 \text{ A}$$

$$CA = i_1 = 2.5 \text{ A}$$

$$AD = i_1 - i_2 = 2.5 - 0.625 = 1.875 \text{ A}$$

Q5) In the given circuit diagram, the currents  $I_1 = -0.3 \text{ A}$ ,  $I_4 = 0.8 \text{ A}$  and  $I_5 = 0.4 \text{ A}$ , are flowing as shown, the current  $I_2$ ,  $I_3$  and  $I_6$  respectively are.

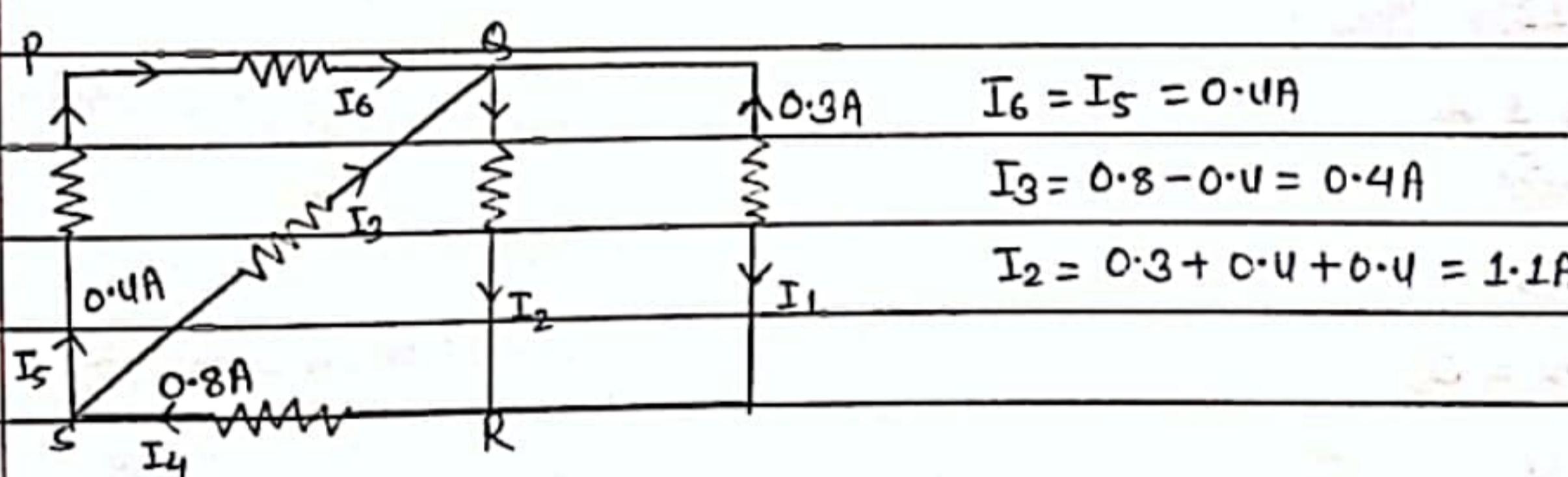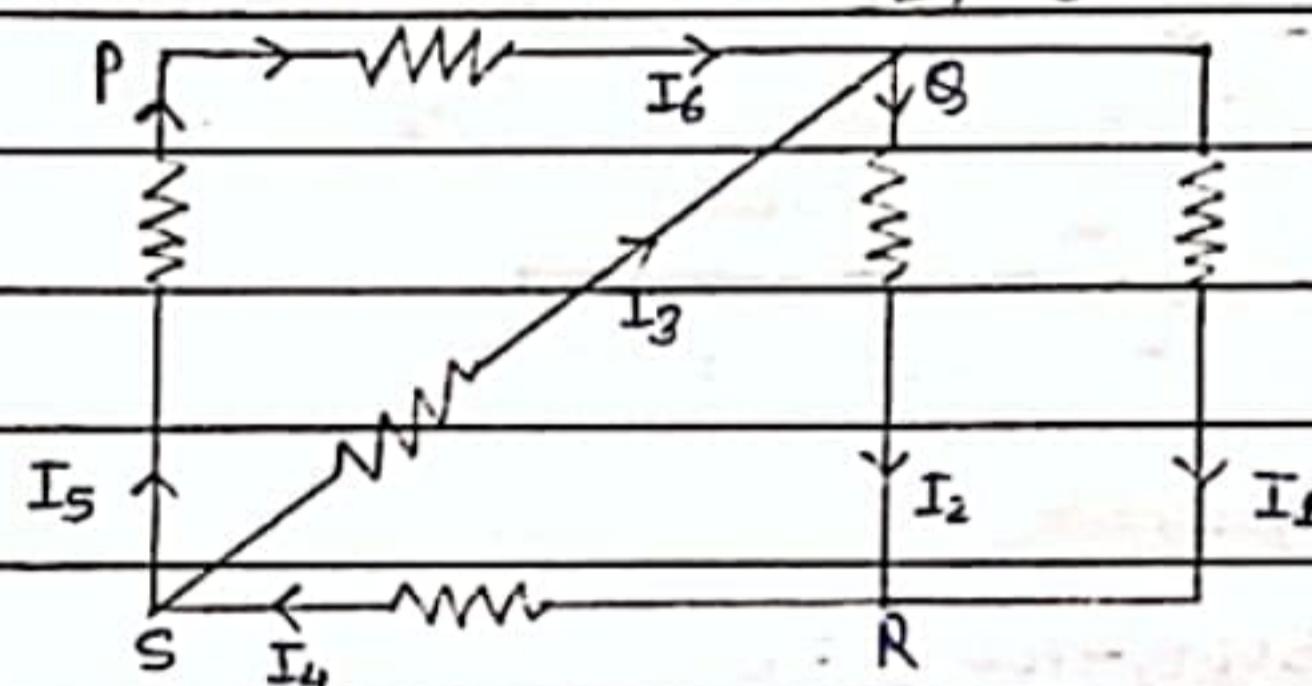- a)  $1.1 \text{ A}, 0.4 \text{ A}, 0.4 \text{ A}$
- b)  $1.1 \text{ A}, -0.4 \text{ A}, 0.4 \text{ A}$
- c)  $0.4 \text{ A}, 1.1 \text{ A}, 0.4 \text{ A}$
- d)  $-0.4 \text{ A}, 0.4 \text{ A}, 1.1 \text{ A}$



Q6) What is the current  $i$ .

a)  $1 \text{ A}$   $\Rightarrow 9 + 2i + i + 2i - 3 + i = 0$


b)  $-1 \text{ A}$   $6i = -6$

c)  $2 \text{ A}$   $i = -1 \text{ A}$

d)  $3 \text{ A}$   $3v + i = 9v$


Q7) In the circuit shown the cells A and B have negligible resistances. For  $V_A = 12V$ ,  $R_1 = 500\Omega$  and  $R = 100\Omega$ , the galvanometer ( $G$ ) shows no deflection. The value of  $V_B$  is:

- a. 4V
- b. 2V
- c. 12V
- d. 6V

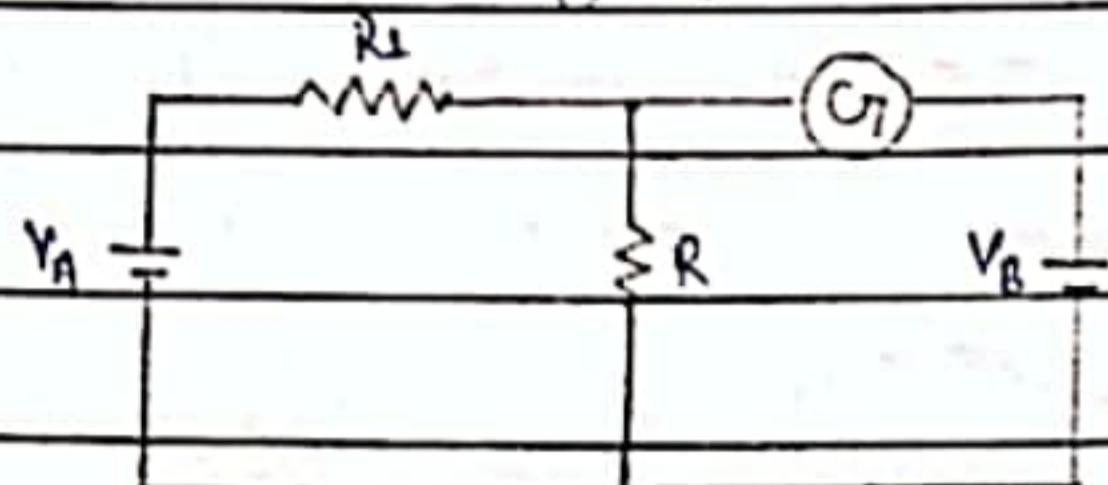

Solution:

$$R_1 = 500\Omega$$

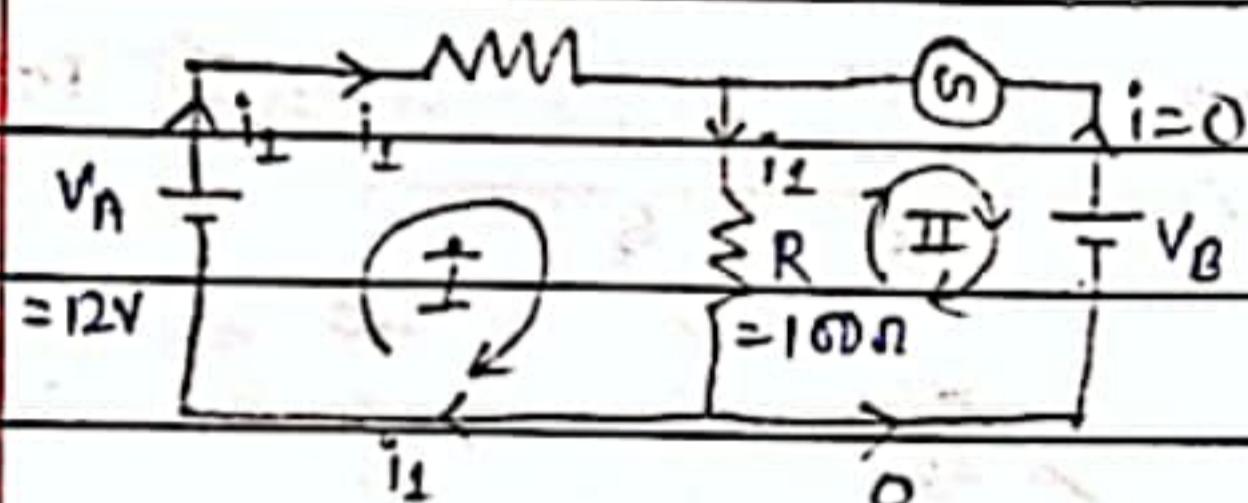

For loop I,

$$12 - 500i_1 - 100i_1 = 0$$

$$600i_1 = 12$$

$$i_1 = \frac{12}{600} = \frac{1}{50} A$$

For loop II,


$$100i_2 - V_B = 0$$

$$V_B = 100i_2$$


$$V_B = 100 \times \frac{1}{50} = 2V$$

Q8) See the electrical circuit shown in the figure. Which of the following equations is a correct equation for it?

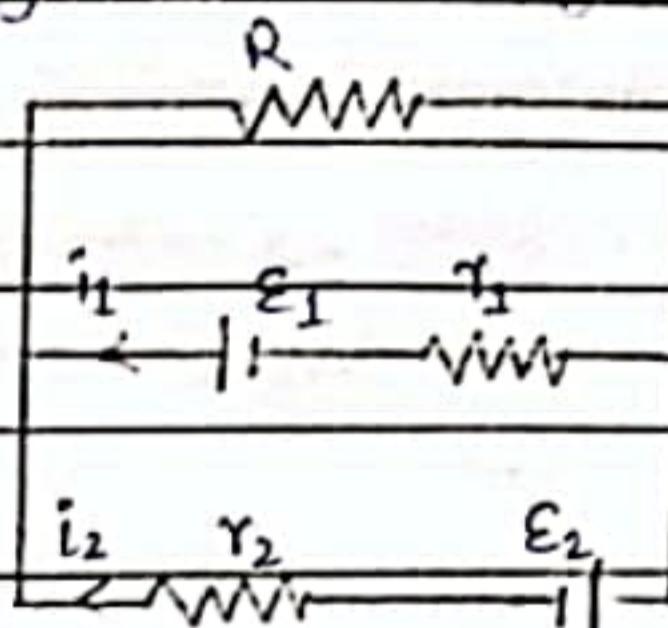- a.  $\mathcal{E}_1 - (i_1 + i_2)R - i_1 r_1 = 0$
- b.  $\mathcal{E}_2 - i_2 r_2 - \mathcal{E}_1 - i_1 r_1 = 0$
- c.  $-\mathcal{E}_2 - (i_1 + i_2)R + i_2 r_2 = 0$
- d.  $\mathcal{E}_1 - (i_1 + i_2)R + i_1 r_1 = 0$




Solution:  $R \quad i_1 + i_2$

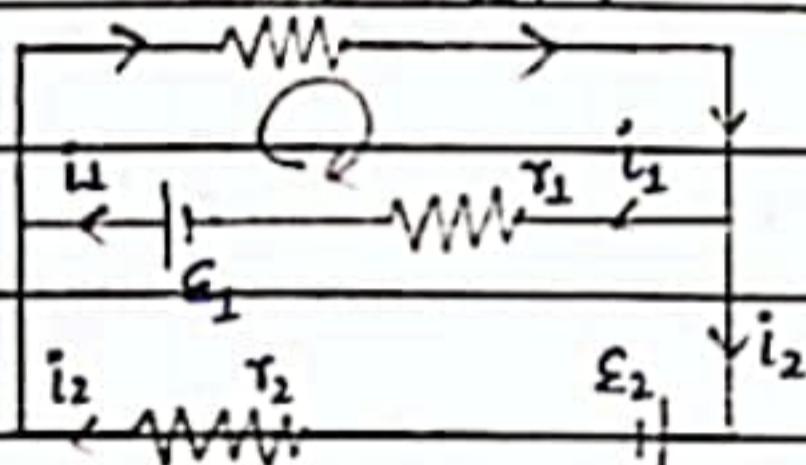


$$\Rightarrow \mathcal{E}_1 - (i_1 + i_2)R - i_1 r_1 = 0$$

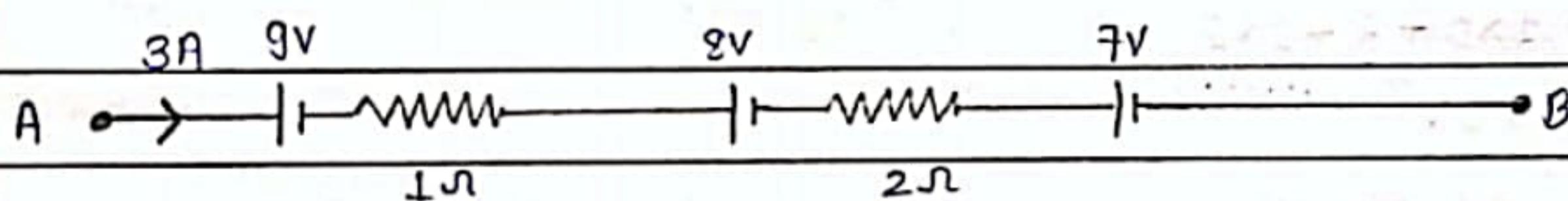Q9) Find the potential difference between A and B ( $V_A - V_B$ ).



- a) 30V
- b) -30V
- c) 33V
- d) -33V


Solution:  $9V$

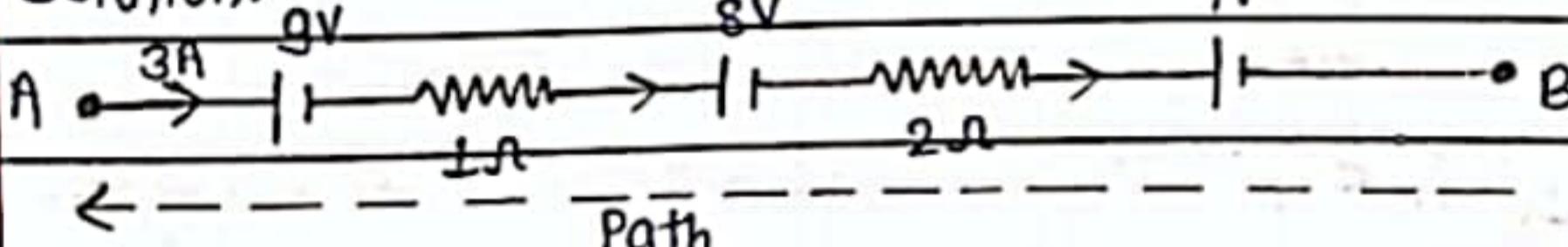

$$V_A - V_B = 7 + 2 \times 3 + 8 + 1 \times 3 + 9$$


$$= 33V$$

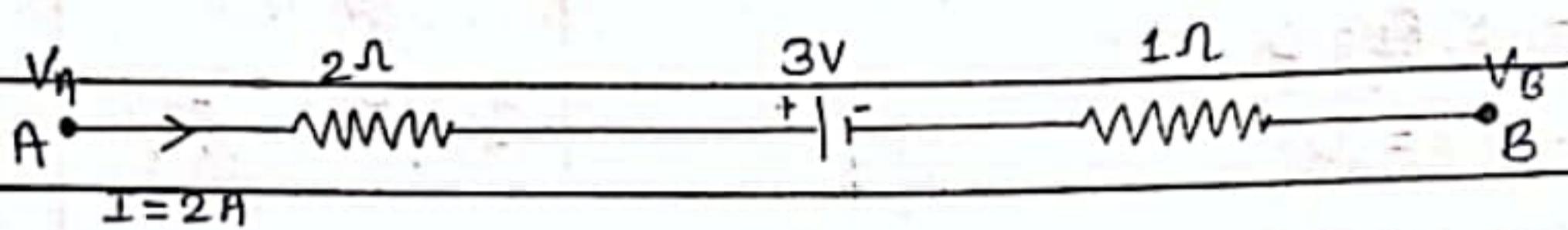Q10) The potential difference ( $V_A - V_B$ ) between the points A and B in the given figure is:



- a) +9V
- b) -3V
- c) +3V
- d) +6V


Solution:

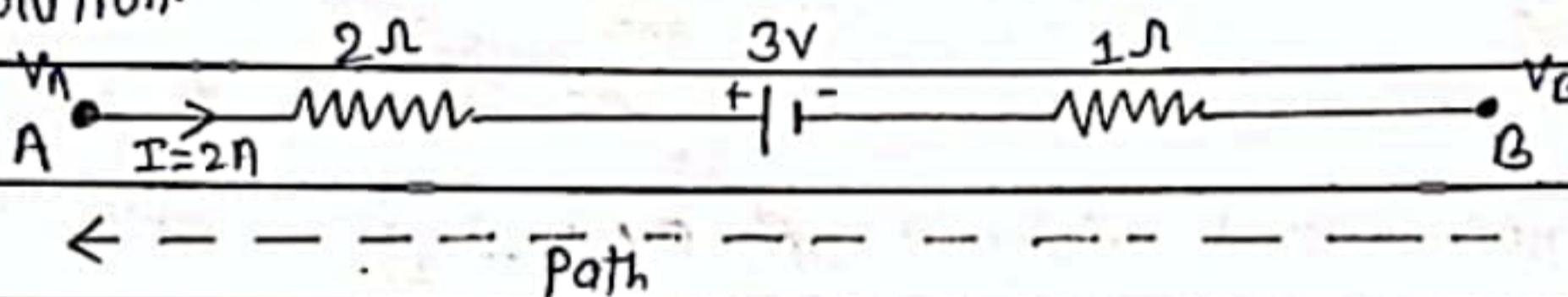


$$V_A - V_B = 1 \times 2 + 3 + 2 \times 2 \\ \therefore +9V$$

Q11) In the circuit shown in the figure, if the potential at point A is taken to be zero, the potential at point B is

- a. -2V
- b. +1V
- c. -1V
- d. +2V

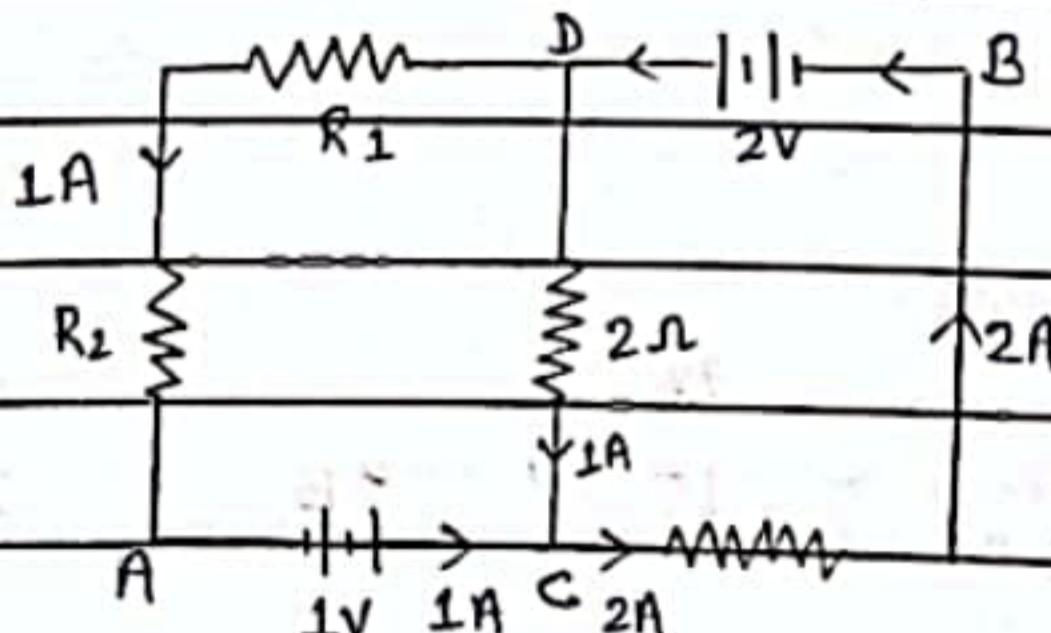

Solution:


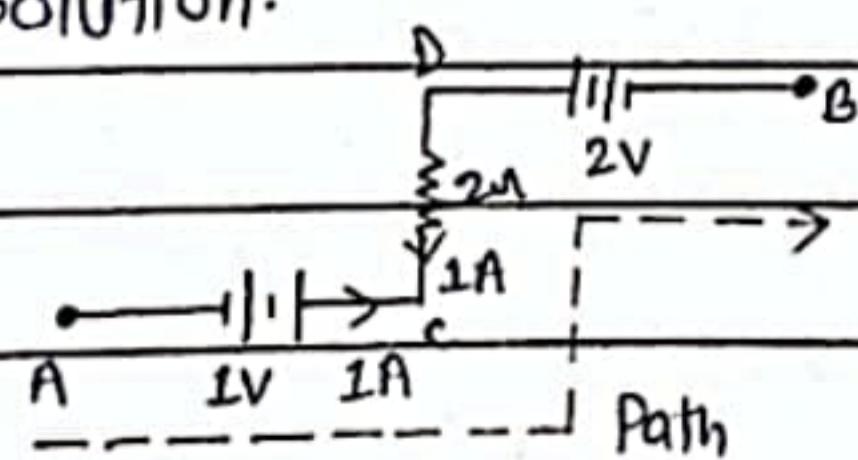


$$1 + 2 - 2 = V_B - V_A$$

$$V_B = +1V$$

Q12) The reading of an ideal voltmeter in the circuit shown is,

- a. 0.4V
- b. 0.6V
- c. 0V
- d. 0.5V

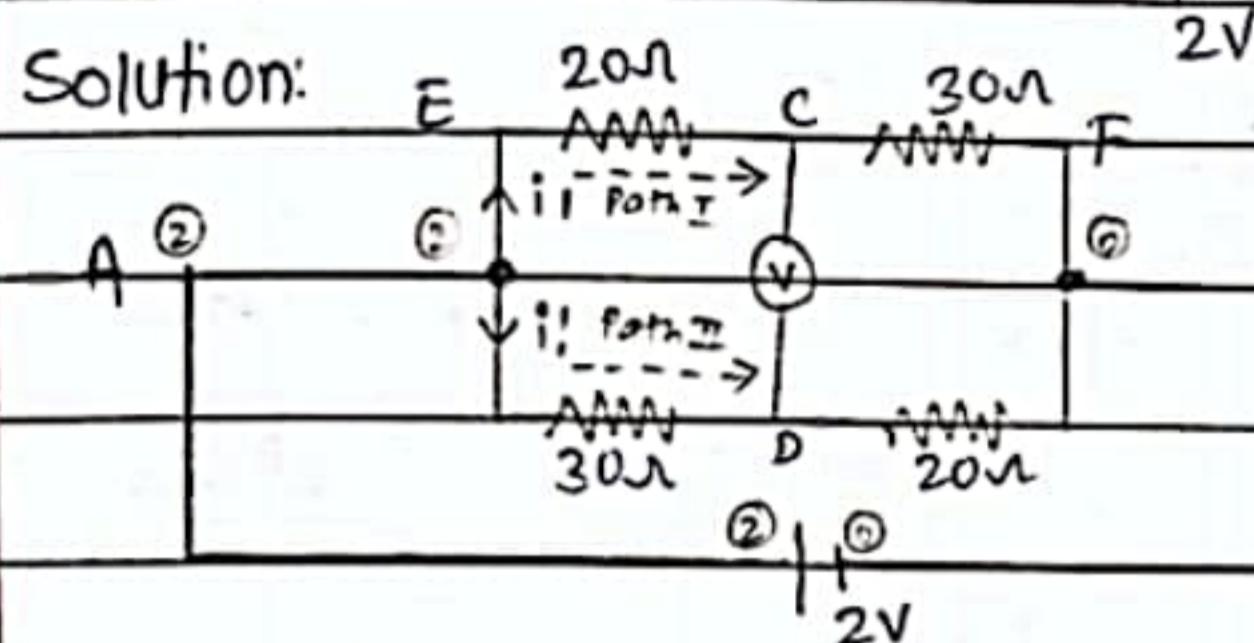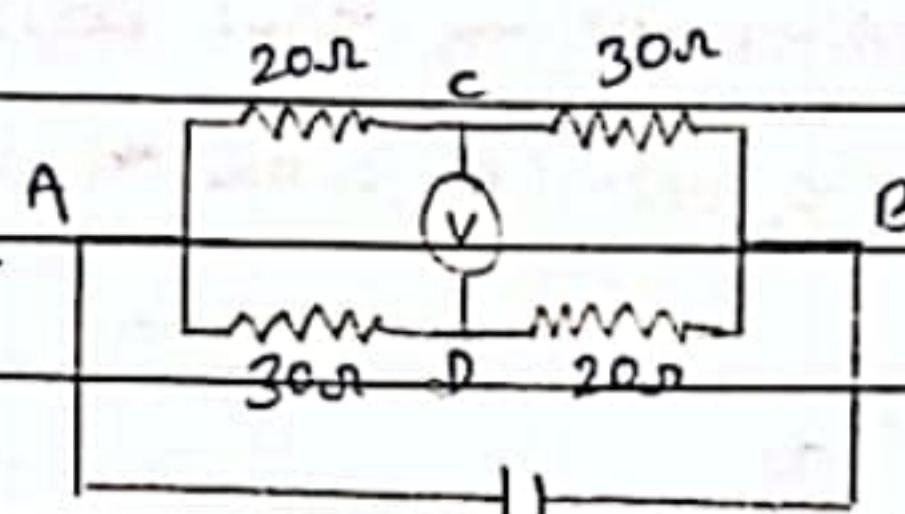

Equivalent Resistance of branch EF ( $R_{eq}$ ) =  $50\Omega$

$$i = \frac{v}{R_{eq}} = \frac{2}{50} A$$

Ideal Voltmeter

$$R \rightarrow \infty$$

$$i = \frac{v}{R} = 0$$

In Path I,

$$V_C - V_A = -20i \quad \text{(i)}$$

No current in

In Path II,

$$V_D - V_A = -30i \quad \text{(ii)}$$

voltmeter branch.

Solving (i) and (ii)

Ideal Ammeter

$$R \rightarrow 0$$

$$V_C - V_D = 10i = 10 \times \frac{2}{50}$$

$$V_C - V_D = 0.4V$$

## \* WHEATSTONE BRIDGE

Wheatstone Bridge is an arrangement of four resistances which can be used to measure one of them in terms of the rest.

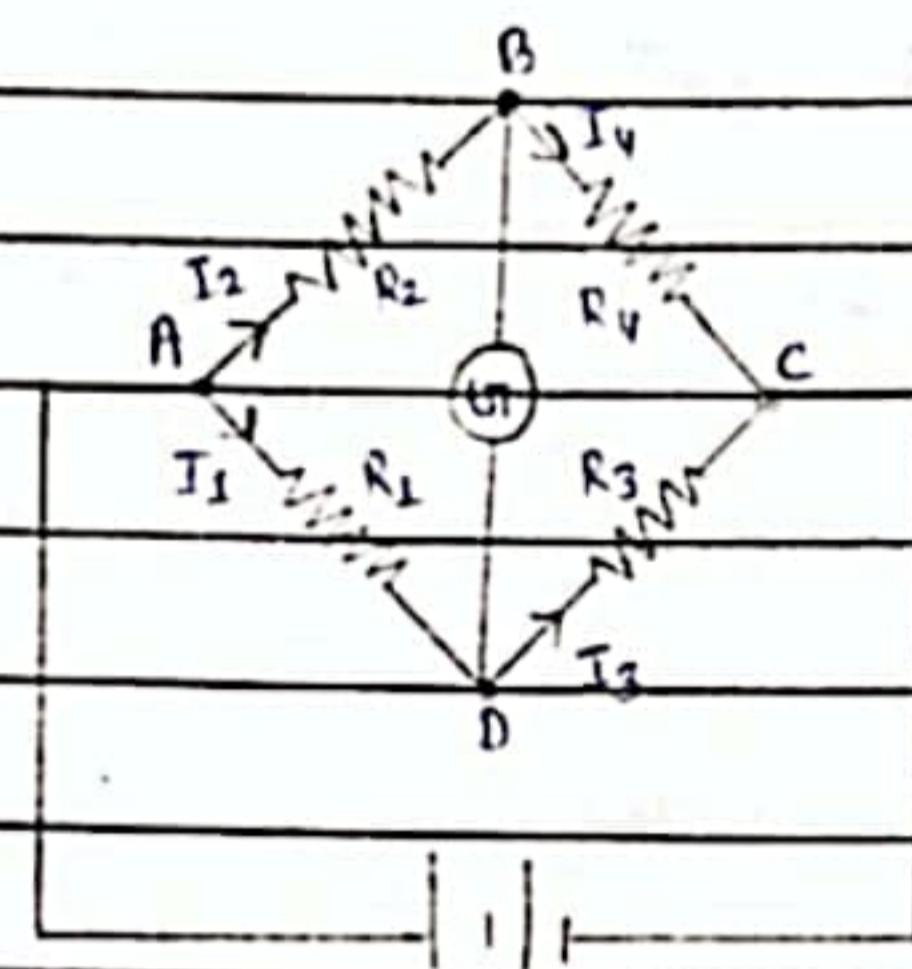


Fig: wheatstone bridge

Assume that the cell has no internal resistance. In general, there will be currents flowing across all branches as well as  $I_g$  through G. Of special interest, is the case of a balanced bridge where the resistors are such that  $I_g = 0$ . In this case,  $I_1 = I_3$  and  $I_2 = I_4$ .

Applying loop law in loop ABDA

$$-I_2 R_2 + 0 + I_1 R_1 = 0$$

$$I_1 R_1 = I_2 R_2$$

$$\frac{I_1}{I_2} = \frac{R_2}{R_1} \quad \text{--- (i)}$$

In loop BCDG.

$$-I_4 R_4 + I_3 R_3 + 0 = 0$$

$$I_3 R_3 = I_4 R_4$$

$$\frac{I_3}{I_4} = \frac{R_4}{R_3} \quad \text{--- (ii)}$$

From (i) and (ii),  $R_2 = R_4$

This equation is called the balance condition for the galvanometer to give zero or null deflection.


Q1) Calculate equivalent resistance between points A and B.

a.  $3/5 \Omega$


b.  $6/5 \Omega$

c.  $9/5 \Omega$

d.  $18/5 \Omega$

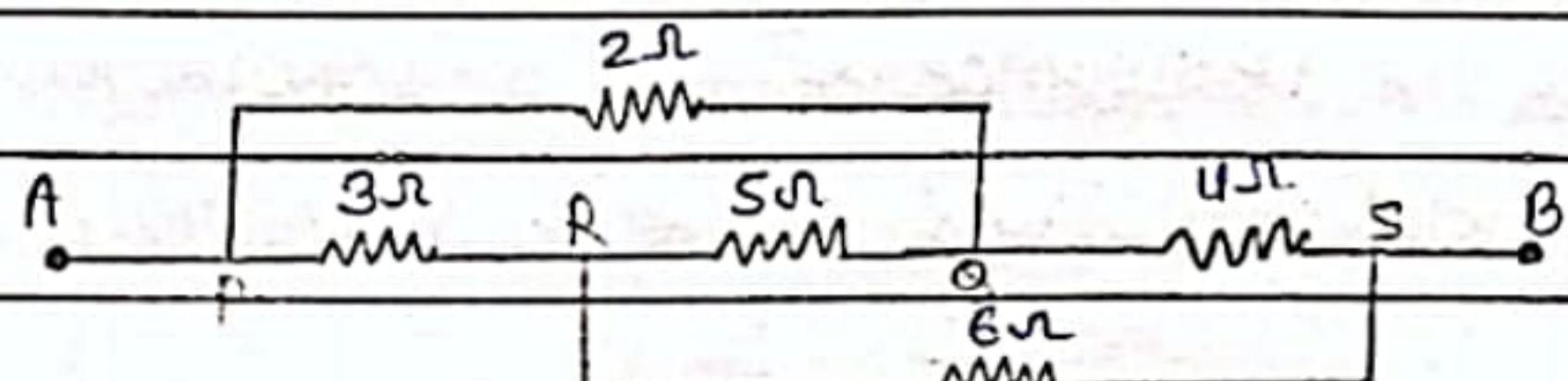

Solution:

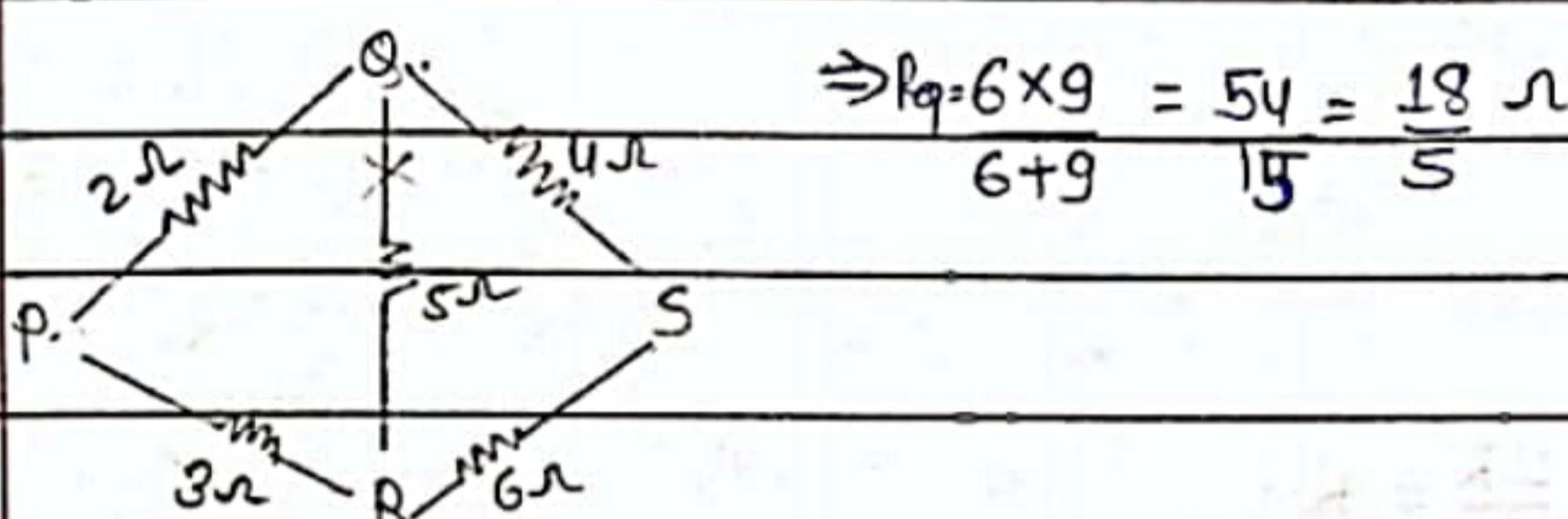


Q2) Calculate equivalent resistance between points A and B.

a.  $r/2$


b.  $r$

c.  $2r$

d.  $4r$

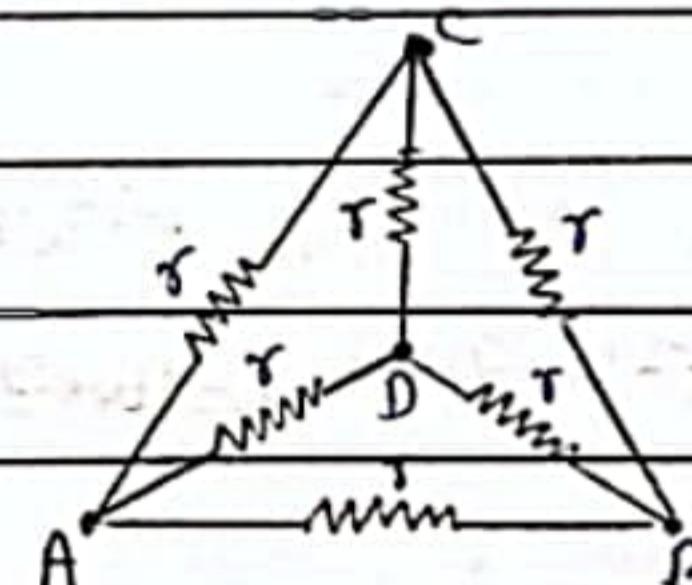

Solution:

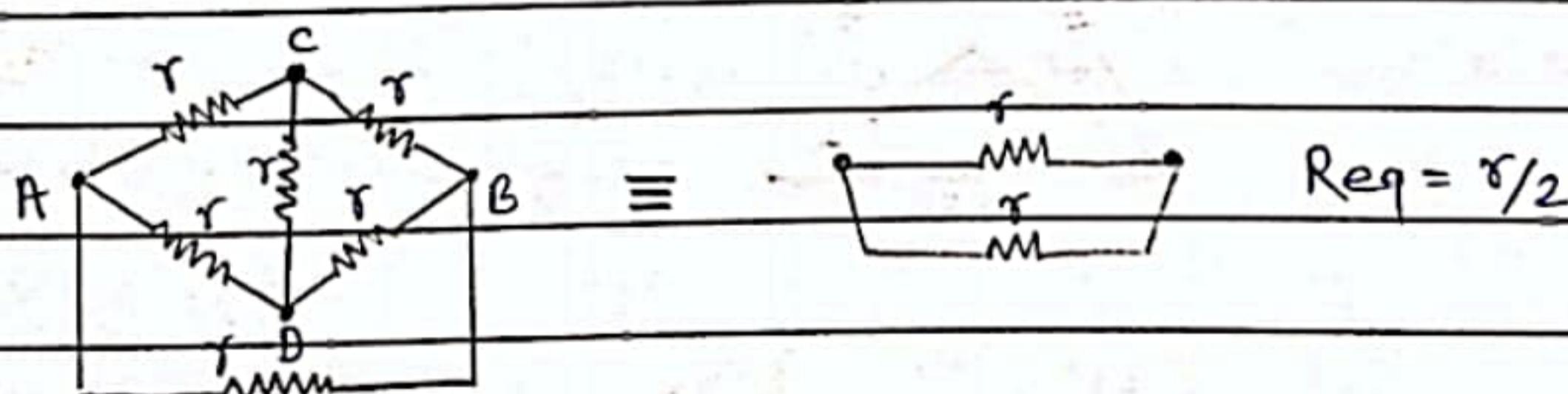


$$R_{\text{eq}} = \frac{3r}{2}$$

Q3)

In a wheatstone bridge, all four arms have equal resistance  $R$ . If the resistance of the galvanometer arm is also  $R$ , the equivalent resistance of the combination as seen by the battery is

- a.  $R/4$
- b.  $R/2$
- c.  $R$
- d.  $2R$ .

Solution:

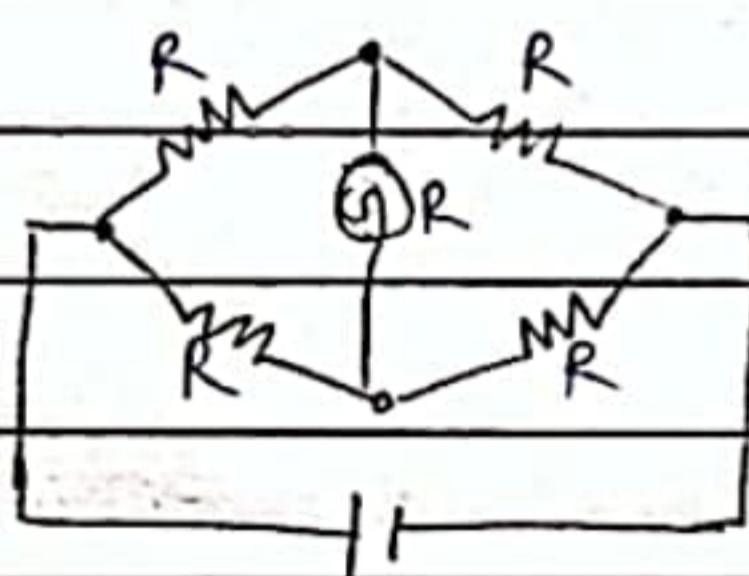


$$R_{eq} = \frac{2R}{2} = R$$


Q4)

In the network shown in the figure each of the resistance is equal to  $2\Omega$ . The resistance between points A and B is

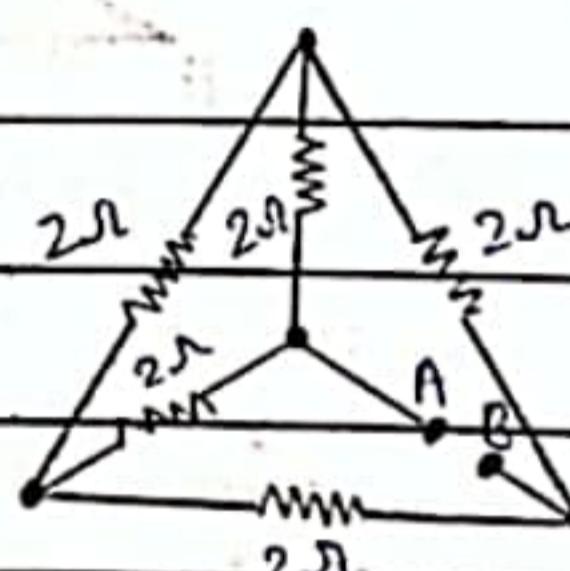- a.  $1\Omega$
- b.  $4\Omega$
- c.  $3\Omega$
- d.  $2\Omega$



Solution:

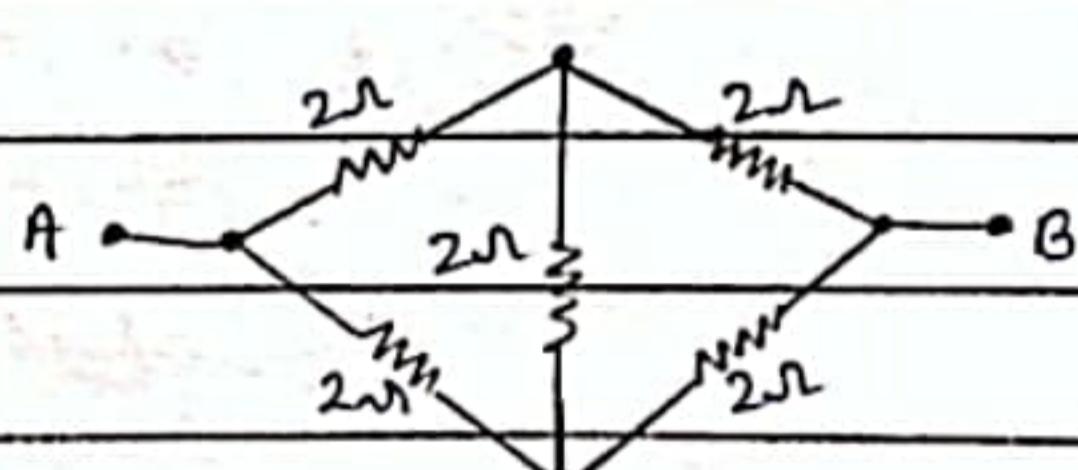


$$R_{eq} = \frac{4}{2} = 2\Omega$$

Q5) Three resistances P, Q, R each of  $2\Omega$  and an unknown resistance S form the four arms of Wheatstone bridge circuit. When a resistance of  $6\Omega$  is connected parallel to S, the bridge gets balanced. What is the value of S?

- |    |    |
|----|----|
| a. | 3л |
| b. | 6л |
| c. | 1л |
| d. | 2л |

### Solutions

Equivalent of  $6\Omega$  and  $S = 6S$

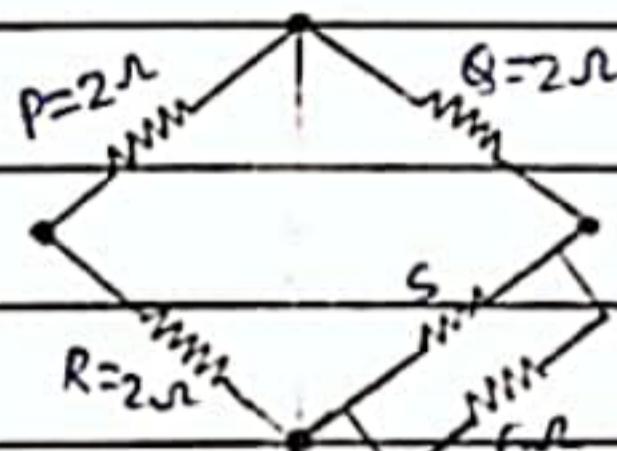

$$\frac{2}{2} = \frac{2}{6+s}$$

$$\text{or, } \frac{6s}{6+s} = 2$$

$$\text{on } \underline{2s} = 6+s$$

$$\alpha \leq 3n$$

Q6) For the network shown in the figure, the value of current is

- a. | g v

- 35


- b. 5v

- 18

- 10

- c. | 5v

- 1

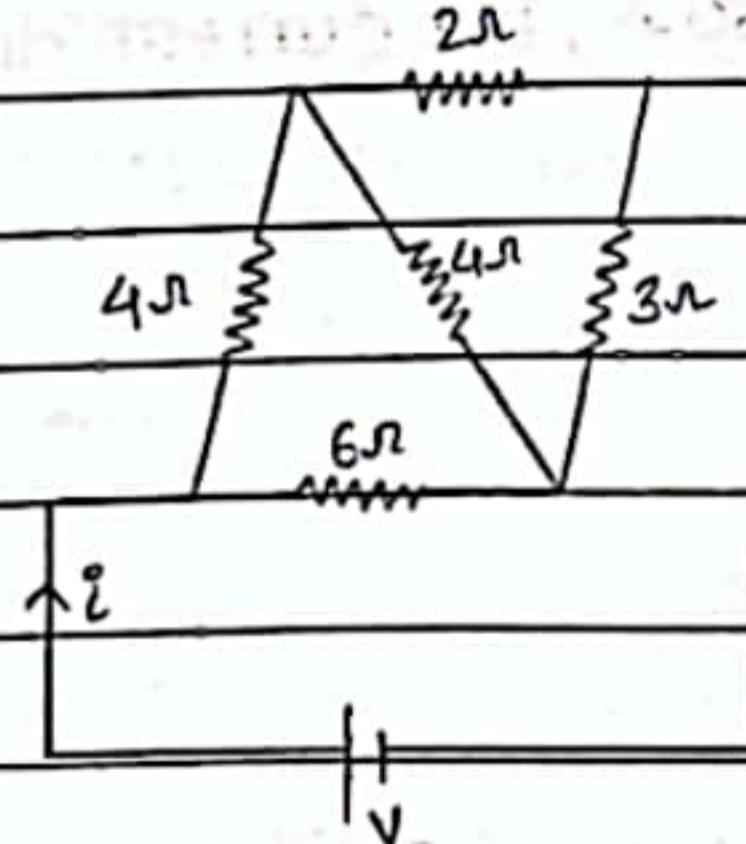


### Solutions


$$Re = \frac{6 \times 9}{6+9} = \frac{54}{15} = 3.6, \quad i = \frac{V}{Re} = \frac{5V}{3.6} = 1.39V$$

Q7.) Five equal resistances each of resistance  $R$  are connected as shown in the figure. A battery of  $V$  volts is connected between A and B. The current flowing in AFCEB will be.

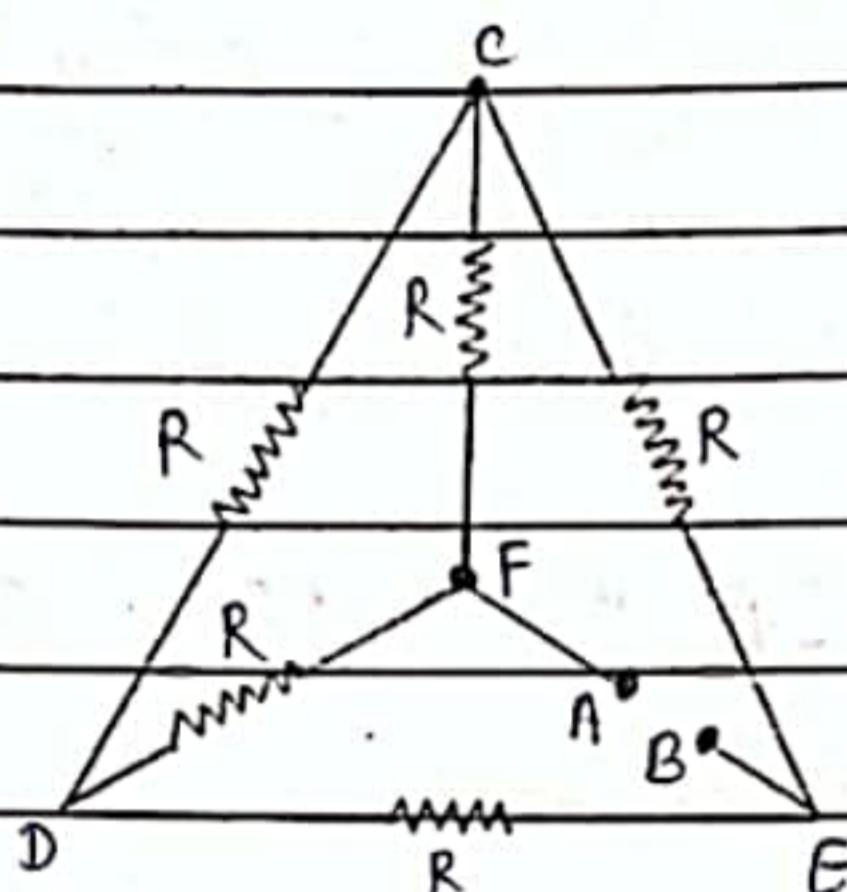- a.  $\frac{3V}{R}$
- b.  $\frac{V}{R}$
- c.  $\frac{V}{2R}$
- d.  $\frac{2V}{R}$




Solution:

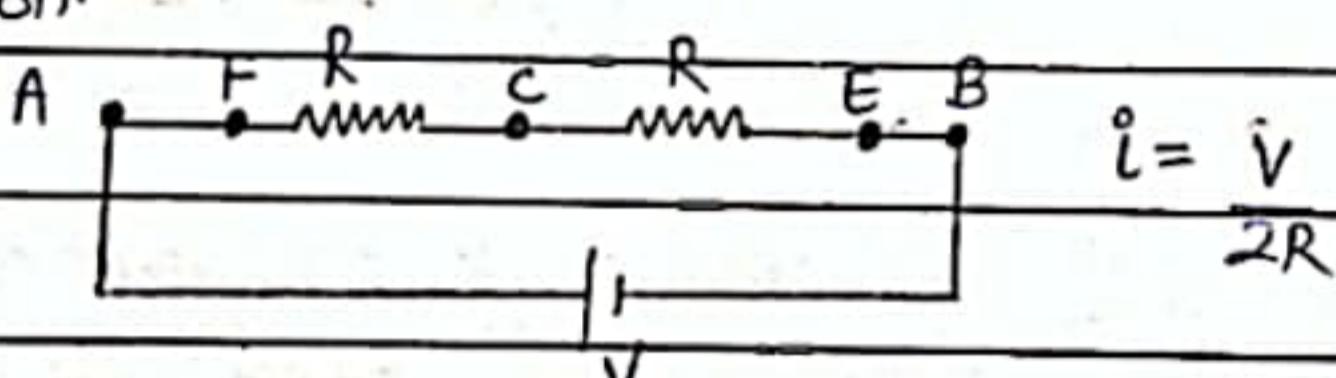

Q8.) The resistance of the four arms P, Q, R and S in a Wheatstone's bridge are  $10\Omega$ ,  $30\Omega$ ,  $30\Omega$  and  $90\Omega$  respectively. The emf and internal resistance of the cell are  $7V$  and  $5\Omega$  respectively. If the galvanometer resistance is  $50\Omega$ , the current drawn from the cell will be

- a. 1.0A
- b. 0.2A
- c. 0.1A
- d. 2.0A

Solution:

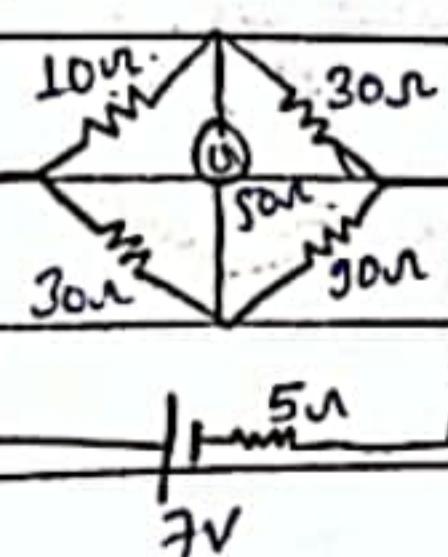

$$R_e = \frac{40 \times 120}{40 + 120} + 5 = 35\Omega$$

$$I = \frac{V}{R_e} = \frac{7}{35} = 0.2A$$

## \* METER BRIDGE

A meter bridge is an electrical instrument based on the principle of a wheatstone bridge that helps in determining the value of unknown resistance.

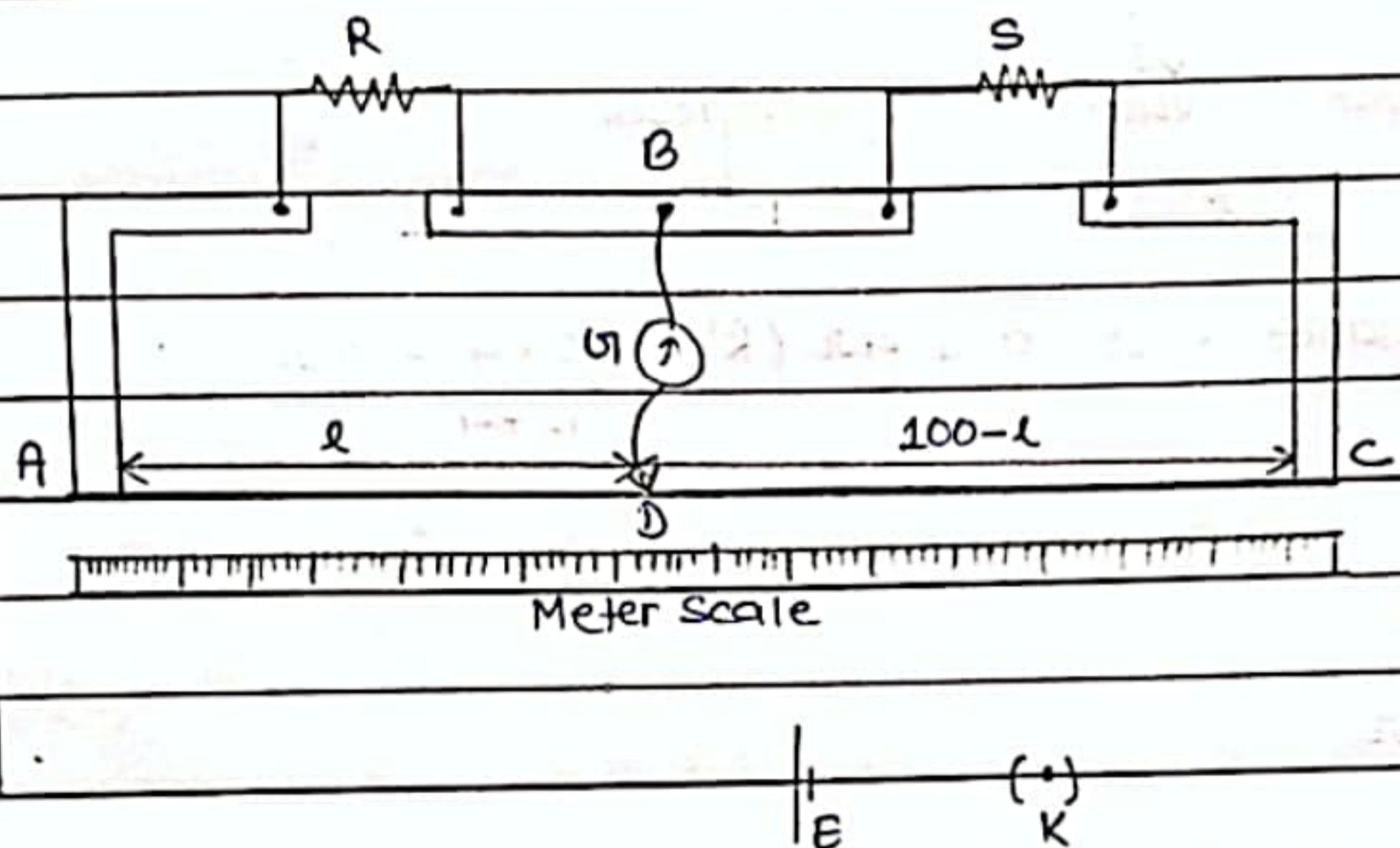


Fig: Meter bridge

In the above diagram,  $R$  is the unknown resistance,  $S$  is the known resistance,  $G$  is galvanometer and  $D$  is the position of jockey as it is made to move along the wire  $AC$  of length 1 meter or 100cm. The jockey is moved till the galvanometer shows zero deflection. This confirms that the wheatstone bridge is balanced.


Let  $\text{r m/cm}$  be the resistance per unit length of wire  $AC$ . Then  
resistance of branch  $AD$  ( $R_{AD}$ ) =  $\gamma l$  and  $DC$  ( $R_{DC}$ ) =  $\gamma(100-l)$ .  
The balanced condition thus gives,

$$\frac{R}{R_{AD}} = \frac{s}{R_{DC}}$$

$$\text{on } \frac{R}{\gamma l} = \frac{s}{\gamma(100-l)}$$

$$\therefore R = s \frac{l}{100-l}$$

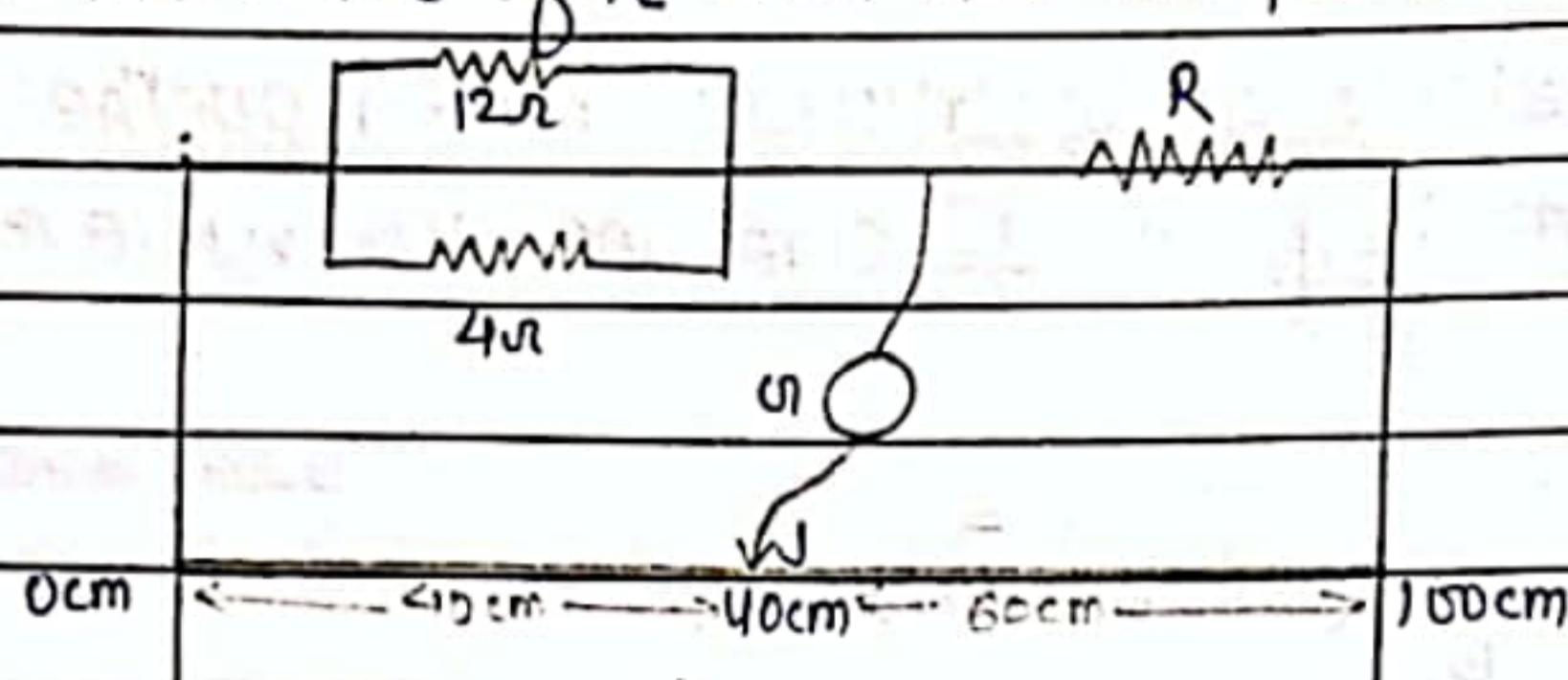Q) Find the value of  $R$  such that null point is at 40cm.




Solution:

$$\text{Equivalent resistance of } 12\Omega \text{ and } 4\Omega (R') = \frac{12 \times 4}{12 + 4} = 3\Omega$$

$$\text{Then, } \frac{3}{40} = \frac{R}{60}$$

$$\text{or } R = \frac{180}{40} = 4.5\Omega$$

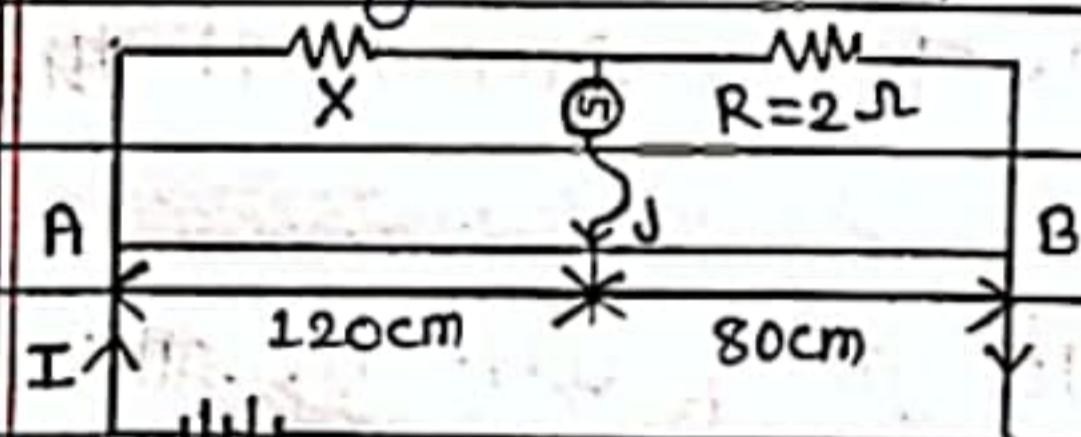Q) Calculate the current and unknown resistance ( $x$ ) if no current flows in the galvanometer as in figure alongside. Assuming resistance per unit length of the wire AB is  $0.01\Omega\text{cm}^{-1}$ .



Solution:

Unknown resistance ( $x$ ) = ?

current ( $I$ ) = ?

$$R = 2\Omega$$

$$l_1 = 120\text{cm}$$

$$l_2 = 80\text{cm}$$

For no galvanometer deflection,

$$\frac{X}{120} = \frac{2}{80}$$

$$\therefore X = 3\Omega$$

Equivalent resistance of  $X$  and  $R(R_1) = 5\Omega$

Total resistance of wire AB ( $R_2$ ) =  $200 \times 0.01$

$$= 2\Omega$$

$$\text{Effective resistance of the circuit } (R) = \frac{5 \times 2}{5+2} = \frac{10}{7} \Omega$$

$$\text{Current } (I) = \frac{4}{10/7} = 2.8A$$

## \* POTENTIOMETER

A potentiometer is an arrangement or a device which does not draw any current from the given circuit and still measures the potential difference or emf of a cell.

A potentiometer measures emf accurately without drawing any current from the cell as this method of measurement follows null deflection.

### Principle:

The voltage drop across the length of the conductor having uniform cross section and composition is directly proportional to its length.

$$V \propto l$$

$$V = k l$$

$k = \frac{V}{l}$  where  $k$  is a constant called potential gradient and is the voltage drop per unit length of the conductor.

### Construction

Potentiometer is basically a uniform wire, sometimes a few meters in length across which a standard cell is connected. In the figure, the wire runs from A to C. The small vertical portions are the thick metal strips connecting the various sections of the wire. A current  $I$  flows through the wire which can be varied by rheostat.


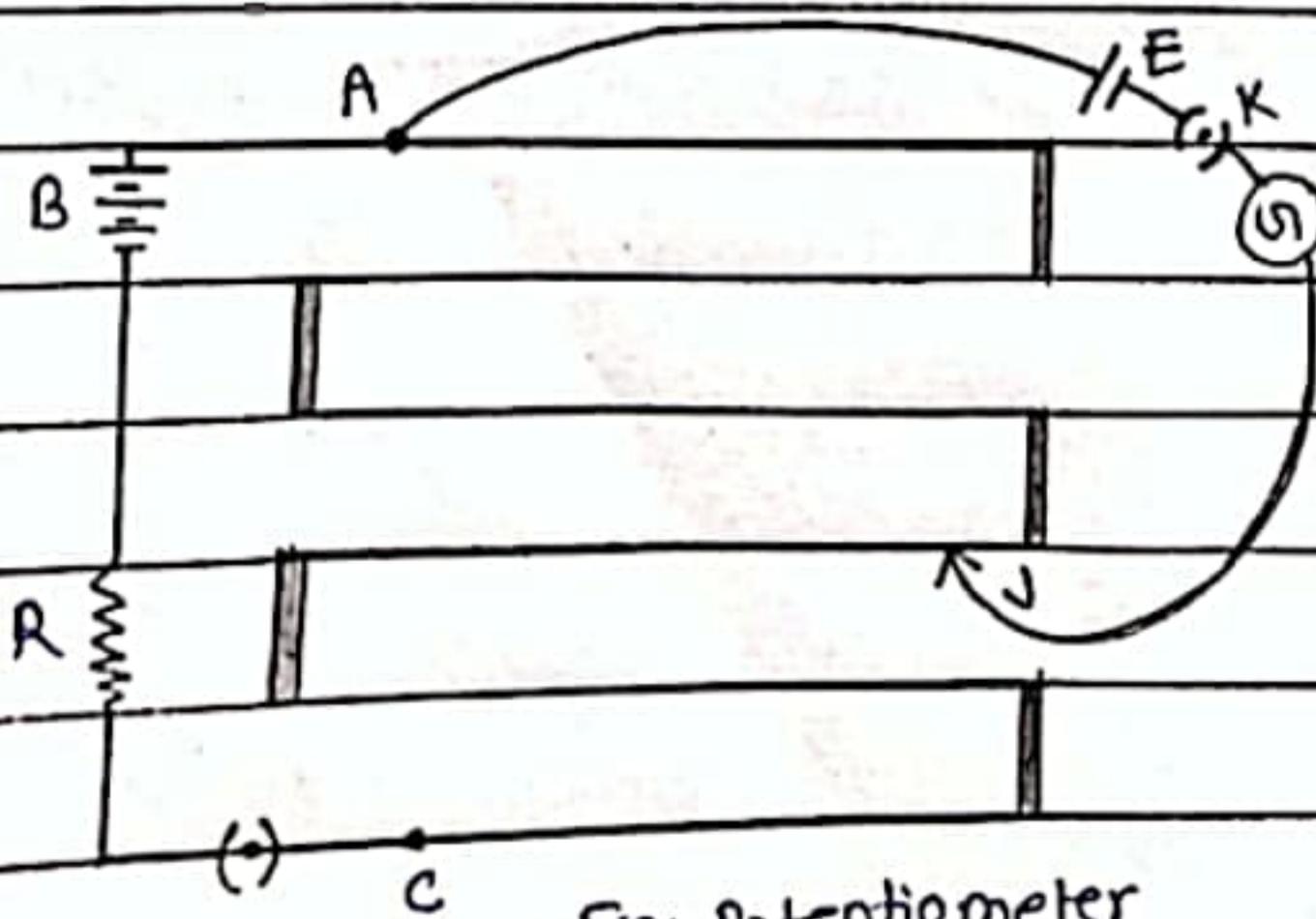


Fig: Potentiometer

## Uses of potentiometer

- Comparison of EMFs of two cells

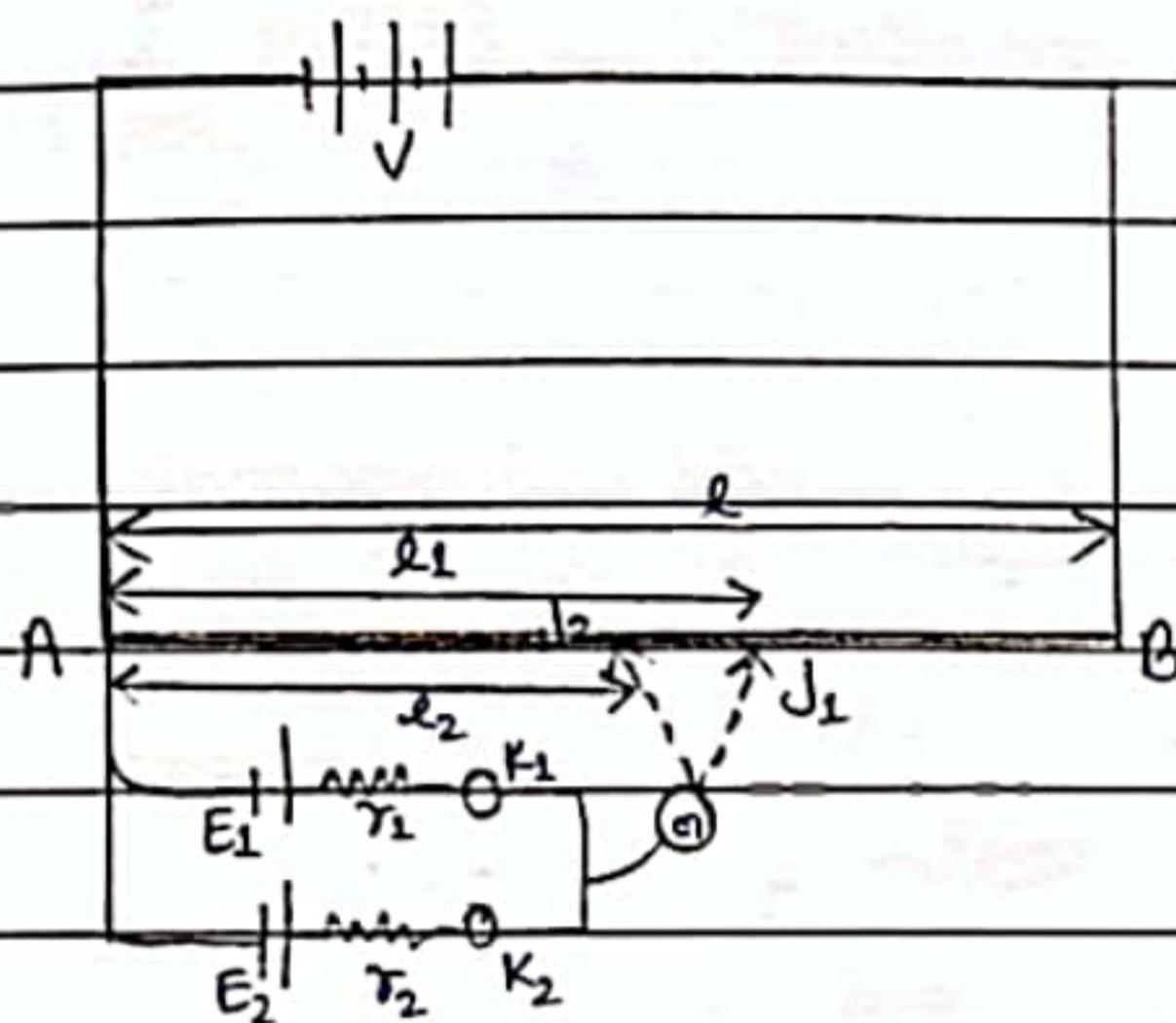

### Note

- \* Polarity must be same
- \* P.d. across potentiometer wire > cell's emf.

If  $K_1$  is closed and  $K_2$  is open, let null deflection is obtained at  $l_1$ .

$$\text{Then, } \frac{V \times l_1}{l} = E_1$$

$$\text{or, } E_1 = K \times l_1 \quad \text{--- (i)}$$

Similarly, if  $K_1$  is open and  $K_2$  is closed, let null deflection is obtained at  $l_2$ . Then;

$$\frac{V \times l_2}{l} = E_2$$

$$\text{or, } E_2 = K \times l_2 \quad \text{--- (ii)}$$


From equations (i) and (ii),

$$E_1 = l_1 \quad \text{--- (iii)}$$

$$E_2 = l_2$$

Equation (iii) can be used to compare the EMFs of two cells by measuring  $l_1$  and  $l_2$ .

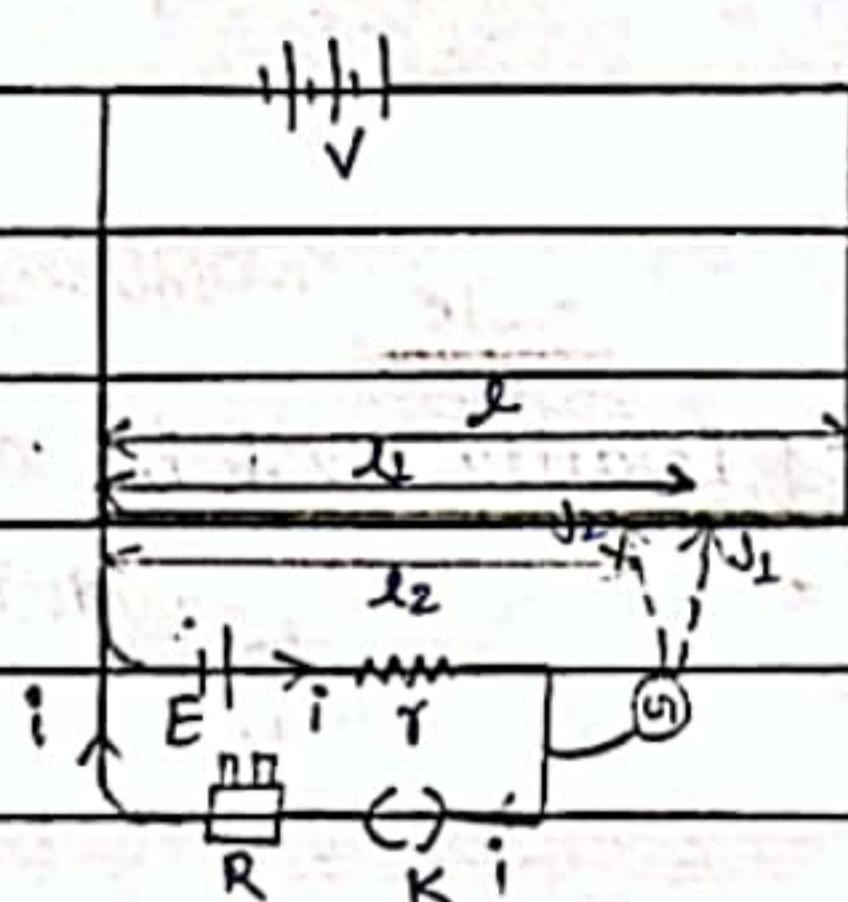- Measurement of Internal resistance of the cell.



From Ohm's law in lower circuit,

$$i = \frac{E}{R+r}$$

If K is open and null deflection point is obtained at length  $l_1$ . Then,

$$\frac{V}{l} \times l_1 = E$$

$$E = kl_1 \quad \text{---(i)}$$

If K is closed and null deflection point is obtained at length  $l_2$ . Then,

$$\frac{V}{l} \times l_2 = E - ir$$

$$\text{or } E - \left(\frac{E}{R+r}\right)r = kl_2$$

$$\text{or } ER + Er - Er = kl_2$$

$$R+r$$

$$\text{or } ER = kl_2 \quad \text{---(ii)}$$

$$R+r$$

From (i) and (ii)

$$l_1 = \frac{E(R+r)}{ER}$$

$$l_2 = \frac{ER}{E(R+r)}$$

$$\text{or, } R+r = \frac{l_1}{l_2}$$

$$R = \frac{l_1}{l_2} - r$$

$$\text{or } r = \frac{R}{l_2} (l_1 - l)$$

$$\text{or } r = R \left( \frac{l_1 - l}{l_2} \right)$$

$\therefore$  The value of internal resistance ( $r$ ) can be calculated by knowing  $R$ ,  $l_1$  and  $l_2$ .

Q) A simple potentiometer circuit is set up as in figure using a uniform wire AB, 1m long, which has a resistance of  $2\Omega$ . The resistance of the 4V battery is negligible. If the variable resistor  $R$  were given a value of  $2.4\Omega$ , what would be the length AC for zero galvanometer deflection?

Solution:

$$E_1 = 4V$$

$$E_2 = 1.5V$$

$$R = 2.4\Omega$$

$$R_{AB} = 2\Omega$$

$$l_{AB} = 1m$$

$$l_{AC} = ?$$

$$\text{Current } (I) = \frac{4}{2.4 + 2} = 0.9A$$

$$\text{Potential drop across AB} = 2 \times 0.9 = 1.8V$$


We know,

$$E_2 = \frac{1.8}{1} l_{AC}$$

$$\therefore 1.5 = l_{AC}$$

$$1.8$$

$$\therefore l_{AC} = 0.825 \text{ m.}$$

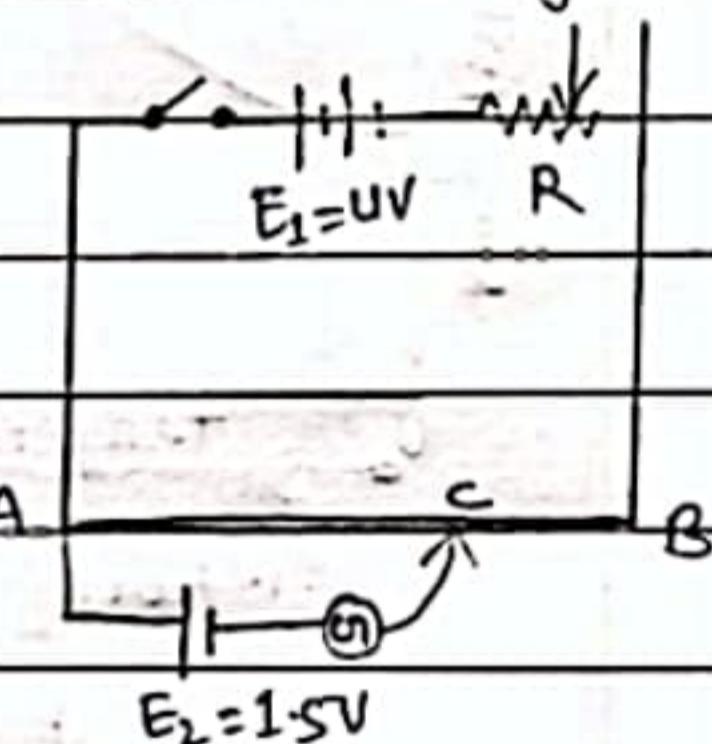

## \* Superconductivity

Certain metals and alloys that acquire infinite conductivity (zero resistivity) at low temperature are superconductors and the property of superconductors is called superconductivity.

The temperature below which the special metal exhibit the superconductivity is called critical temperature ( $T_c$ ).

The variation of resistivity on changing temperature for normal metals and superconductors are shown below:

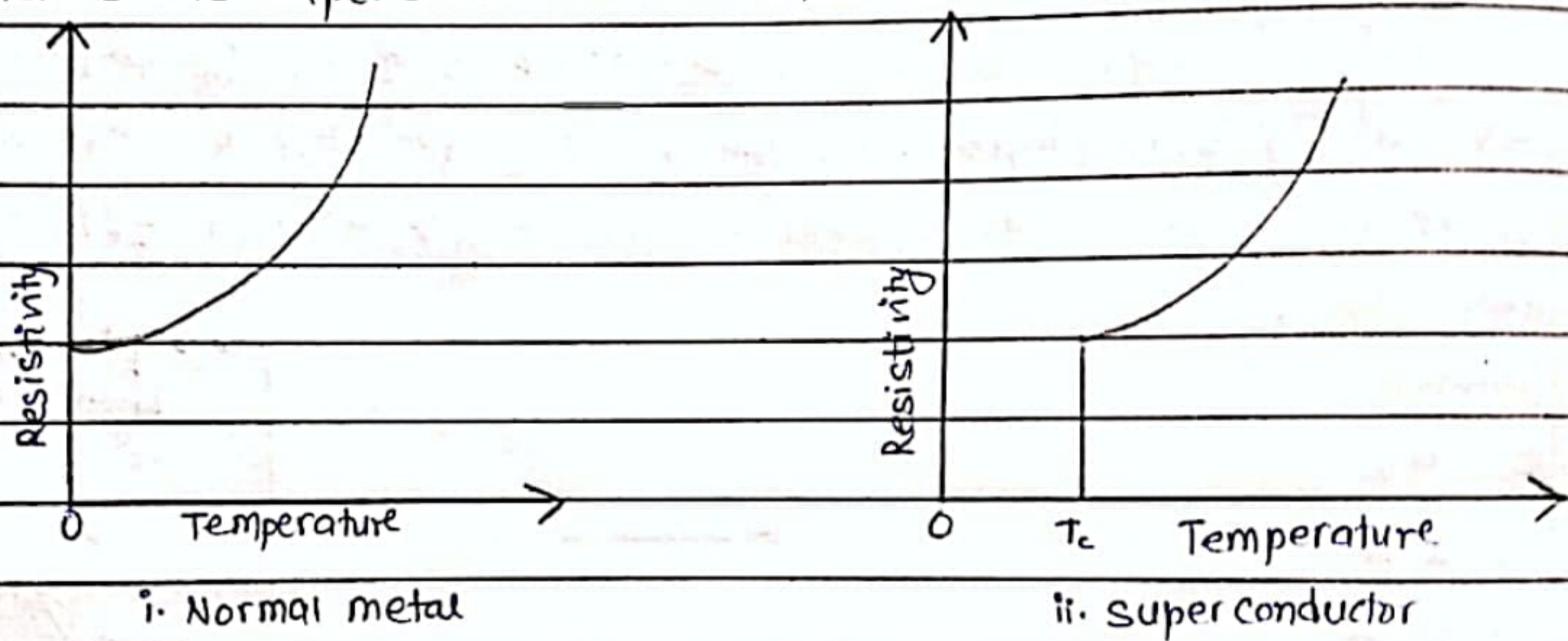


Fig: Resistivity vs temperature graph

The magnetic lines of force are pushed out from superconductors when placed in the magnetic field. This effect is called Meissner effect.

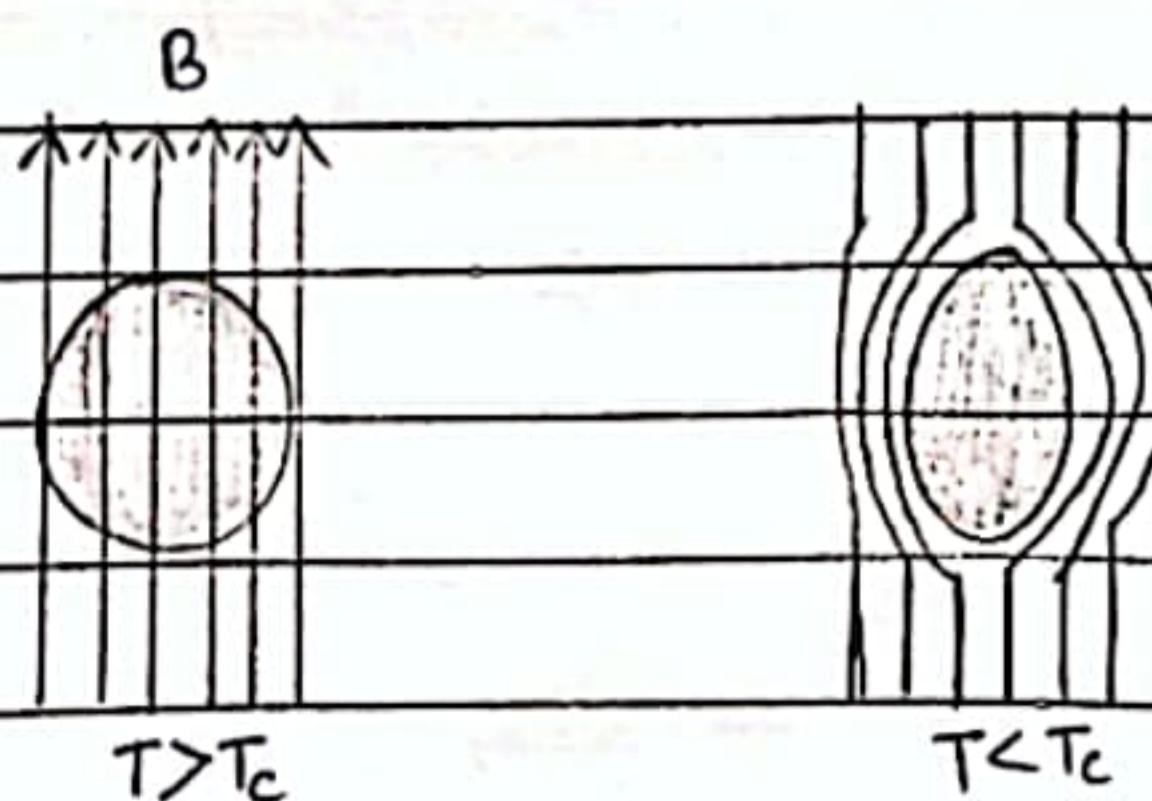


Fig: Meissner effect

## Perfect Conductors

Perfect conductors are ideal conductors having zero resistivity.

## Differences between perfect conductors and superconductors

Perfect conductors	Superconductors
Magnetic field inside the perfect conductor has non zero value.	Magnetic field inside the superconductor is zero.
They don't show Meissner effect.	They show Meissner effect.
Temperature should be decreased to 0K to get a perfect conductor.	Superconductors can be made above 0K, below critical temperature.

## \* Electrical Devices

### 1. Voltmeter

A voltmeter is an electrical device which is used to measure the electric potential difference between two points in an electric circuit. A voltmeter is connected in parallel with a device to measure the voltage drop across it.

### 2. Ammeter

An ammeter is an electrical device which is used to measure the electric current in a circuit. It is connected in series with the circuit.

### 3. Galvanometer

Galvanometer is an electrical device which detects the presence of current in a circuit. It is denoted in circuit by  $\textcircled{G}$ .

Shunt: A very small resistance connected in parallel to the galvanometer is called a shunt. It is denoted by S. It serves to reduce the internal resistance of an ammeter.

Multiplier: A very high resistance connected in series to the galvanometer is called a multiplier. It is denoted by  $R$ . It serves to increase the internal resistance of a voltmeter.

### i) Conversion of a galvanometer into an ammeter

To convert a galvanometer into an ammeter, a very low resistance i.e. shunt is connected in parallel with galvanometer coil so that maximum current can flow through it. Shunt provides an alternative path for excess current.

Let,  $s$  be the value of shunt resistance,  $g$  be the galvanometer resistance,  $i$  be the total current through the circuit and  $i_g$  be the maximum current through the galvanometer which gives full scale deflection in it and  $(i - i_g)$  be the remaining current passing through the shunt

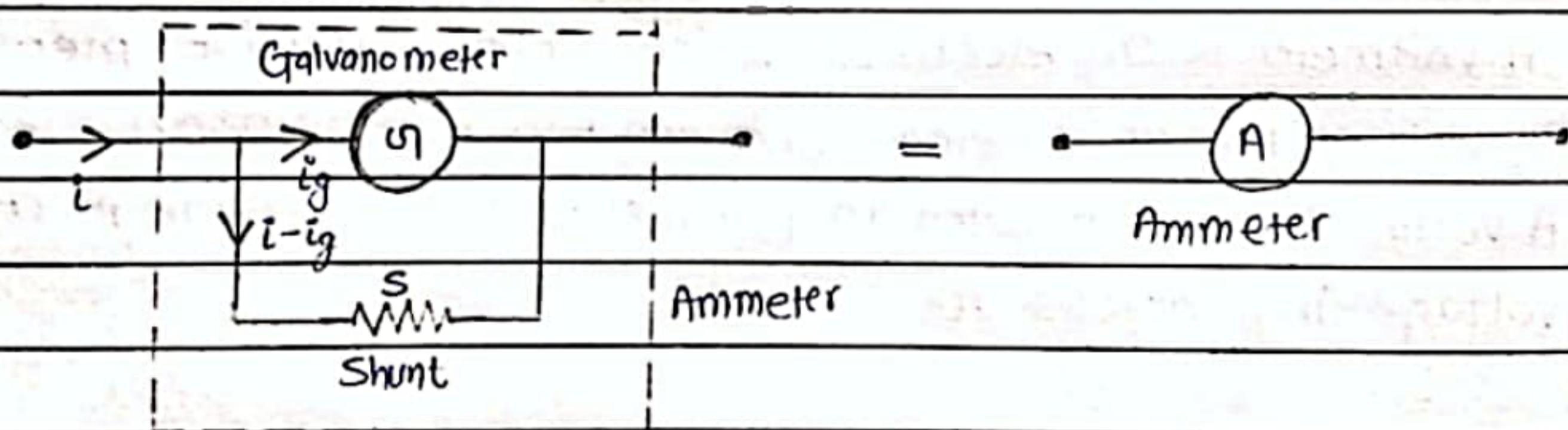


Fig: conversion of galvanometer into ammeter

As the galvanometer and shunt are connected parallel to each other,  
Potential difference across galvanometer = Potential difference across shunt

$$\text{i.e. } i_g g = (i - i_g)s$$

$$\therefore s = \left( \frac{i_g}{i - i_g} \right) g$$

This gives the required value of shunt which when connected in parallel with galvanometer coil to convert galvanometer into ammeter

### Internal Resistance of Ammeter

The equivalent resistance of ammeter is,

$$R = \frac{S\Omega}{S+\Omega} \text{ which is even smaller than the resistance of the shunt (S).}$$

(8) A galvanometer coil whose coil resistance is  $10\Omega$  gives full scale deflection for  $5mA$ . How can you convert it into an ammeter of range  $0-5A$ ?

Solution:

$$n = 10\Omega$$

$$i_g = 5mA = 5 \times 10^{-3}A$$

$$i = 5A$$

$$S = ?$$

Now,

$$S = \left( \frac{i_g}{i - i_g} \right) n$$

$$= \left( \frac{5 \times 10^{-3}}{5 - 5 \times 10^{-3}} \right) \times 10$$

$$= 0.01\Omega$$

∴ It can be converted into an ammeter of range  $0-5A$  by connecting a shunt of  $0.01\Omega$  in parallel with galvanometer coil.

Q) A galvanometer whose coil resistance is  $1\Omega$  has 50 divisions which measures  $1\mu A$  per division. How can you convert it into an ammeter of range  $0-10A$ ?

Solution:

$$G = 1\Omega$$

$$\text{No. of divisions } (n) = 50$$

$$I_g = 1\mu A \times 50 = 50\mu A = 50 \times 10^{-6} A$$

$$I = 10A$$

$$S = ?$$

Now,

$$\begin{aligned} S &= \left( \frac{I_g}{I - I_g} \right) G \\ &= \left( \frac{50 \times 10^{-6}}{10 - 50 \times 10^{-6}} \right) \times 1 \\ &= 5 \times 10^{-6} \Omega \end{aligned}$$

$\therefore$  It can be converted into an ammeter of range  $0-10A$  by connecting a shunt of  $5 \times 10^{-6} \Omega$  in parallel with galvanometer coil.

## ii. Conversion of a galvanometer into voltmeter

To convert a galvanometer into voltmeter, a very high resistance i.e. multiplier is connected in series with galvanometer coil so that minimum current can flow through it.

Let,  $R$  be the value of multiplier resistance,  $g$  be the galvanometer resistance,  $i$  be the total current through the circuit and  $i_g$  be the maximum current through the galvanometer which gives full scale deflection in it.

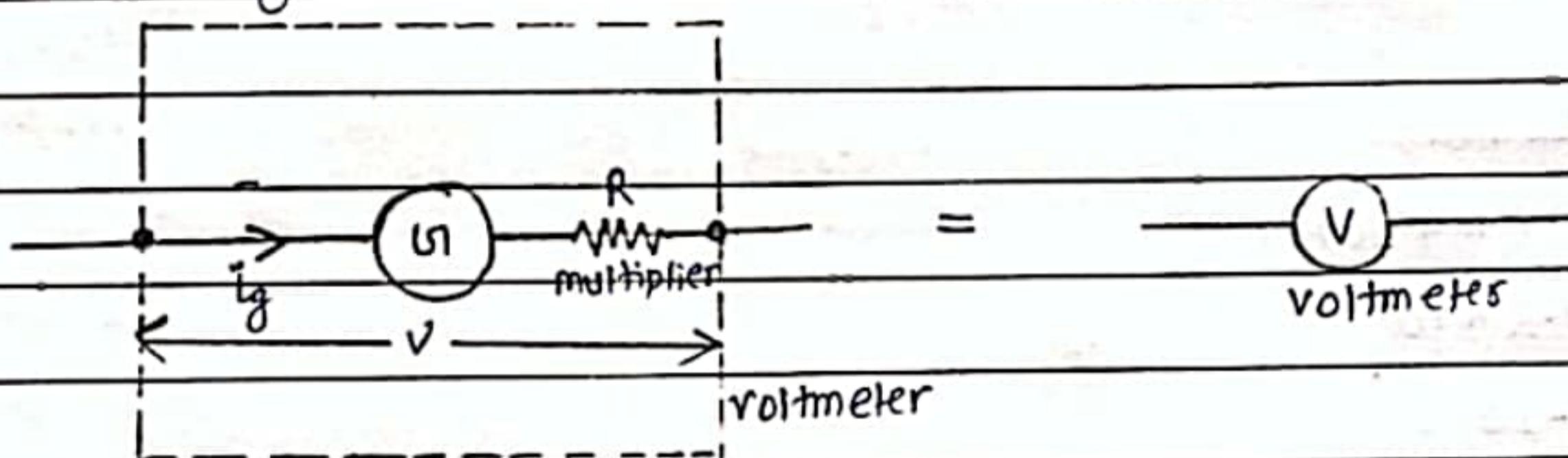


Fig: conversion of galvanometer into voltmeter.

The potential difference ( $V$ ) of the combination of  $g$  and  $R$  is:

$$V = i_g(g + R)$$

$$\text{or, } g + R = \frac{V}{i_g}$$

$$\text{or, } R = V - g$$

This gives the required value of multiplier which when connected in series with galvanometer coil to convert galvanometer into voltmeter.

### • Internal Resistance of Voltmeter.

The equivalent resistance of voltmeter is

$R_v = R + g$  which is greater than the resistance of multiplier. The internal resistance is considered infinity in an ideal voltmeter.

Q) A galvanometer whose coil has resistance  $10\Omega$  gives full deflection for 1mA. How can you convert it into a voltmeter of range 0-2.5V?

Solution:

$$I_g = 10\Omega$$

$$I_g = 1\text{mA} = 1 \times 10^{-3} \text{A}$$

$$V = 2.5 \text{V}$$

$$R = ?$$

Now,

$$V = I_g (R + R_g)$$

$$\text{or } 2.5 = 10^{-3} (R + 10)$$

$$\text{or } R + 10 = 2.5 \times 10^3$$

$$\text{or } R = 2500 - 10$$

$$\therefore R = 2490\Omega$$

$\therefore$  It can be converted into a voltmeter of range 0-2.5V by connecting a multiplier of  $2490\Omega$  in series with galvanometer coil.

#### 4. Ohmmeter

An ohmmeter is an electrical instrument that measures electrical resistance.

## \* Joules Law of Heating

According to Joules Law of heating, the amount of heat ( $H$ ) developed in an ohmic conductor by passage of current is

- directly proportional to the square of current flowing through the conductor.

$$H \propto I^2 \quad \text{--- (i)}$$

- directly proportional to the resistance of the conductor

$$H \propto R \quad \text{--- (ii)}$$

- directly proportional to the time of current flow

$$H \propto t \quad \text{--- (iii)}$$

From (i), (ii) and (iii),

$$H \propto I^2 RT \quad \text{--- (iv)}$$

$H = K I^2 R T$  where  $K$  is the proportionality constant. Its value depends on the system of unit of heat.

- In calorie,  $K = 1$

$$\text{J} \quad \text{--- (v)}$$

Here,  $J$  is the unit conversion factor whose value is  $4.2 \text{ J/calorie}$ . It is also called mechanical equivalent of heat. It is not a physical quantity.

From (iv),

$$H = \frac{I^2 R T}{J} \quad (\text{calorie})$$

- In SI unit,  $K = 1$ . So,

$$H = I^2 R t \quad (\text{Joule})$$

## Experimental Verification of Joule's Law

The experimental arrangement for the verification of Joule's law is as shown in the figure where a battery, a Rheostat, an ammeter, a key and a resistance wire are connected in series.

The wire is immersed in insulated water through which current is passed and the thermometer is used to record the temperature of water.

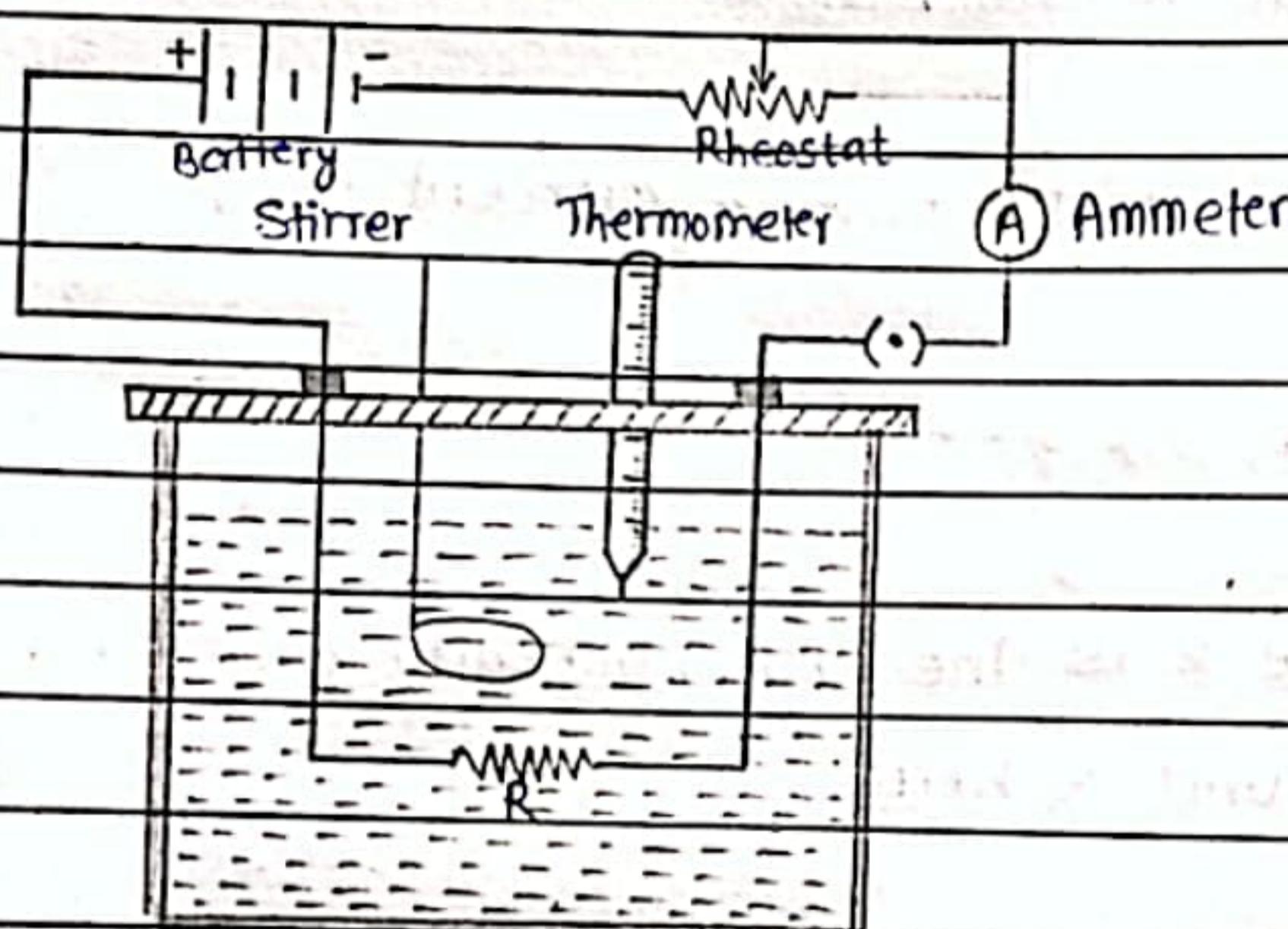



Fig: Experimental arrangement for verification of Joules Law

At first when the key is closed, current flows in the circuit and the heat is produced in the wire and the temperature of the wire rises. The raise in temperature is directly proportional to amount of heat produced.

- i. To verify  $H \propto I^2$  (at constant R and t)

Different magnitude of current ( $I_1, I_2, I_3, \dots$ ) is passed for same time with the help of rheostat. The raise in temperature and their corresponding amount of heat produced ( $H_1, H_2, H_3, \dots$ ) are noted. Then, experimentally it is found that

$$\frac{H_1}{I_1^2} = \frac{H_2}{I_2^2} = \frac{H_3}{I_3^2} = \text{constant}$$

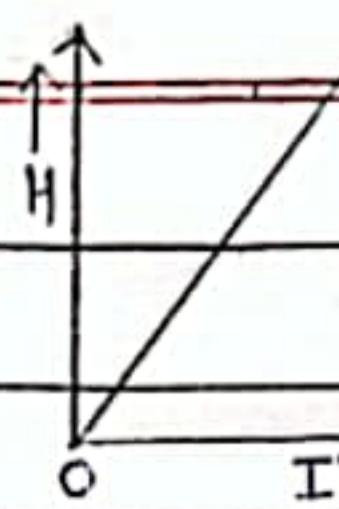Fig: Graph of  $H$  versus  $I^2$ 

$$\therefore H = \text{constant}$$

$$I^2$$


$$\therefore H \propto I^2 \quad \text{--- (i)}$$

ii. To verify  $H \propto R$  (at constant  $I$  and  $t$ )

The experiment is repeated for the wire of same material and diameter but of different length. When the current is passed through the wire, the heat is produced and temperature of water raises. It is found that the amount of heat produced is directly proportional to length. As resistance of wire is directly proportional to length, the amount of heat produced ( $H_1, H_2, H_3, \dots$ ) is proportional to resistance ( $R_1, R_2, R_3, \dots$ ).

$$\frac{H_1}{R_1} = \frac{H_2}{R_2} = \frac{H_3}{R_3} = \text{constant}$$

$$\frac{H}{R} = \text{constant}$$

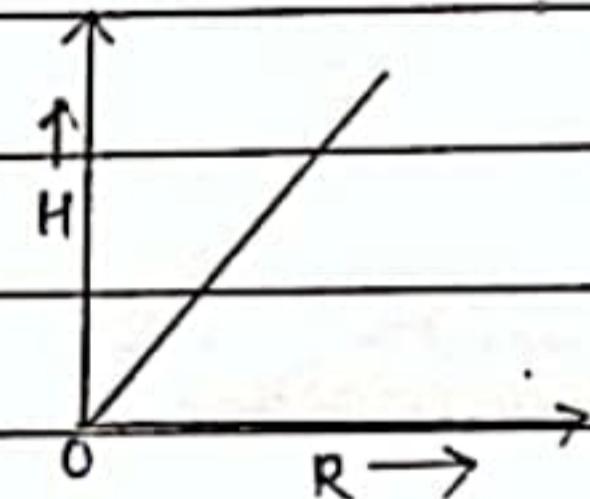
Fig: Graph of  $H$  versus  $R$ 

iii. To verify  $H \propto t$  (at constant  $I$  and  $R$ )

The experiment is repeated for the wire of same length and same amount of current is passed for different time. In this case, we observe that the amount of heat produced ( $H_1, H_2, H_3, \dots$ ) is directly proportional to the time ( $t_1, t_2, t_3, \dots$ ) for which the current is passed.

$$\frac{H_1}{t_1} = \frac{H_2}{t_2} = \frac{H_3}{t_3} = \text{constant}$$

$$\frac{H}{t} = \text{constant}$$

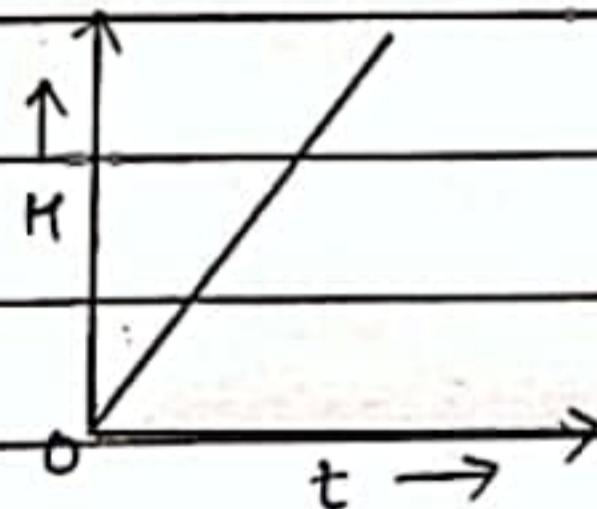Fig: Graph of  $H$  versus  $t$ 

Combining equations (i), (ii) and (iii), we get

$$H \propto I^2 R t$$

$$H = I^2 R t$$

Thus, Joules law is verified.